

ECE113|BASIC ELECTRONICS

Dr. S.S.Jamuar

Lab_5:

Student Name : Shivam Agarwal

Roll No. : 2020123


Date : 31/7/2021

AIM 1 : To draw the phasor diagram of a series RLC circuit and compare the experimental and theoretical results.

Components Used : voltage source ,resistor ,inductor, capacitor , wires.

Software used : LTspice

Circuit Diagram

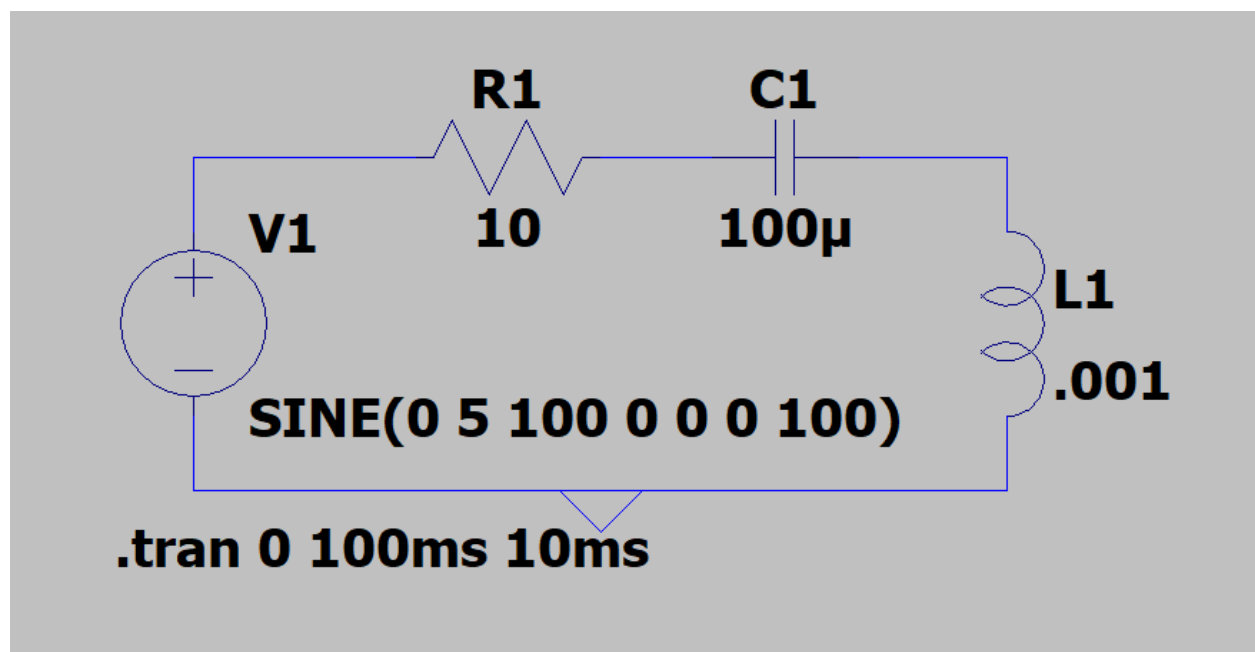

Theoretical calculations(for ideal inductor) :

1) For $f = 100\text{Hz}$

For frequency = 100 Hz.

$$\omega = 2\pi f = 2\pi \cdot 100 = 628.$$

$$R = 10\Omega, L = 0.001\text{H}, C = 100\mu\text{F}.$$

B.

$$X_L = j\omega L = j(0.628)\Omega.$$

$$X_C = -j\frac{1}{\omega C} = -j\left(\frac{1 \times 10^6}{628 \times 100}\right) \\ = -j(15.923)\Omega.$$

$$Z = R + X_L + X_C$$

$$= 10 - j(15.29)$$

$$= 18.27 \angle -56.81^\circ \Omega$$

$$\phi = -56.81^\circ$$

$$I = \frac{V}{Z} = \frac{5 \angle 0^\circ}{18.27 \angle -56.81^\circ}$$

$$= 0.273 \angle 56.81^\circ \text{ A}$$

$$I_{\text{RMS}} = \frac{0.273}{\sqrt{2}} \angle 56.81^\circ \text{ A}$$

$$= 0.193 \angle 56.81^\circ \text{ A}$$

$$V_L = \cancel{I} \cdot I \cdot X_L = I \cdot j\omega L$$

$$= |I\omega L| \angle 90^\circ$$

$$= 0.273 \times (0.628) \angle 90^\circ$$

$$= 0.1714 \angle 90^\circ \text{ V}$$

$$V_{L_{RMS}} = \frac{0.1714}{\sqrt{2}} \angle 90^\circ$$

$$= 0.1212 \angle 90^\circ$$

$$V_C = \cancel{I} \cdot I \cdot X_C = I \left(\frac{-j}{\omega C} \right)$$

$$= 0.273 (15.923) \angle -90^\circ$$

$$= 4.346 \angle -90^\circ \text{ V}$$

$$V_{C_{RMS}} = \frac{4.346}{\sqrt{2}} \angle -90^\circ$$

$$= 3.07 \angle -90^\circ$$

$$V_R = R \cdot I$$

$$= 2.73 \angle 56.81^\circ$$

$$V_{R_{RMS}} = \frac{2.73}{\sqrt{2}} \angle 56.81^\circ$$

$$= 1.93 \angle 56.81^\circ \text{ V}$$

2) For $f = 500\text{Hz}$

$$\text{frequency } (f) = 500\text{Hz}$$

$$\omega = 2\pi(500)$$

$$= 6.28 \times 500 = 3140$$

$$R = 10\Omega, L = 0.001\text{H}, C = 100\mu\text{F}$$

$$X_L = j\omega L = j(3.14)\Omega$$

$$X_C = -j \frac{1}{\omega C} = \frac{-j 10^4}{3140} = -j(3.18)$$

$$Z = R + X_L + X_C$$

$$= 10 - j(0.04)\Omega$$

$$= 10 \angle -0.229^\circ$$

$$= 10 \angle -0.229^\circ \Omega$$

$$\phi = -0.229$$

$$I = \frac{V}{Z} = \frac{5 \angle 0^\circ}{10 \angle -0.229^\circ}$$

$$= 0.5 \angle 0.229^\circ \text{A}$$

$$\cancel{I_{\text{RMS}}} = \cancel{0.353}$$

$$I_{\text{RMS}} = 0.353 \angle 0.229^\circ \text{A}$$

$$V_L = I j\omega L = |I\omega L| \angle 90^\circ$$

$$= 1.57 \angle 90^\circ \text{V}$$

$$V_{L\text{RMS}} = \frac{1.57 \angle 90^\circ}{\sqrt{2}}$$

$$= 1.11 \angle 90^\circ$$

$$V_C = I \left(\frac{-j}{\omega C} \right) = \frac{I}{\omega C} \angle -90^\circ$$

$$= 1.59 \angle -90^\circ$$

$$V_{C_{RMS}} = \frac{1.59}{\sqrt{2}} \angle -90^\circ$$


$$= 1.124 \angle -90^\circ$$

$$V_R = I \cdot R = 5 \angle 0.229^\circ$$

$$V_{R_{RMS}} = \frac{5}{\sqrt{2}} \angle 0.229^\circ$$

$$V_{R_{RMS}} = \frac{5}{\sqrt{2}} \angle 0.229^\circ$$

$$= 3.53 \angle 0.229^\circ$$

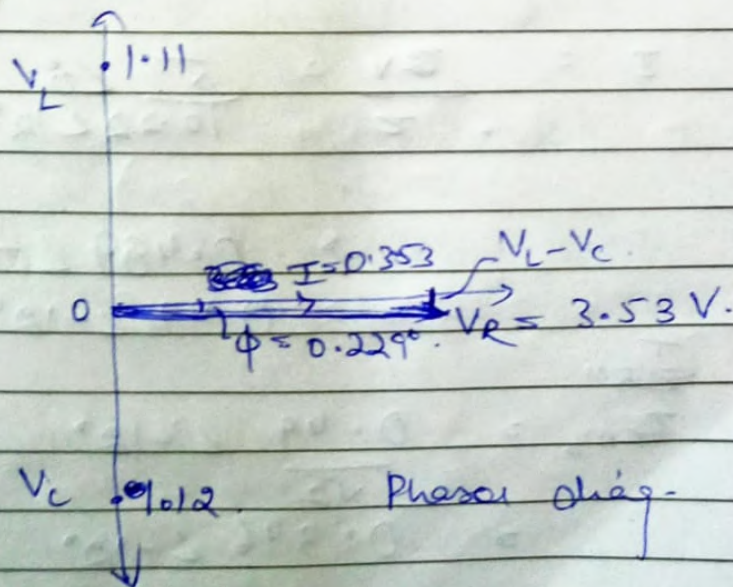

3) For $f = 700 \text{ Hz}$

$$\text{Frequency } (f) = 700 \text{ Hz.}$$

$$\omega = 2\pi(700) = 4396$$

$$R = 10 \Omega, L = 10^{-3} \text{ H}, C = 10^{-4} \text{ F.}$$

$$X_L = j\omega L = j(4.396)$$

$$\begin{aligned} X_C &= -j \frac{1}{\omega C} = -j \left(\frac{10^4}{4396} \right) \\ &= -j(2.274) \end{aligned}$$

$$Z = 10 + j(2.12) \Omega.$$

$$= 10.22 \angle 12^\circ.$$

$$\phi = 12^\circ.$$

$$I = \frac{V}{Z} = \frac{5 \angle 0^\circ}{10.22 \angle 12^\circ}$$

$$= 0.489 \angle -12^\circ.$$

$$\approx 0.49 \angle -12^\circ$$

~~I_{RM}~~

$$I_{RMS} = \frac{0.49 \angle -12^\circ}{\sqrt{2}}$$

$$= 0.346 \angle -12^\circ.$$

$$V_L = I X_L = (0.49)(4.396) \angle 90^\circ$$

$$= 2.15 \angle 90^\circ \text{ V}$$

$$V_{L_{RMS}} = \frac{2.15}{\sqrt{2}} \angle 90^\circ$$

$$= 1.52 \angle 90^\circ \text{ V}$$

$$V_C = I X_C = (0.49)(2.274) \angle -90^\circ$$

$$= 1.11 \angle -90^\circ \text{ V}$$

$$V_{C_{RMS}} = \frac{1.11}{\sqrt{2}} \angle -90^\circ$$

$$= 0.787 \angle -90^\circ \text{ V}$$

$$V_R = I R$$

$$= 4.9 \angle -12^\circ$$


$$V_{R_{RMS}} = \frac{4.9}{\sqrt{2}} \angle -12^\circ$$

$$= 3.46 \angle -12^\circ \text{ V}$$

Practical observations(ideal inductor):


1) For 100 Hz frequency:

For V

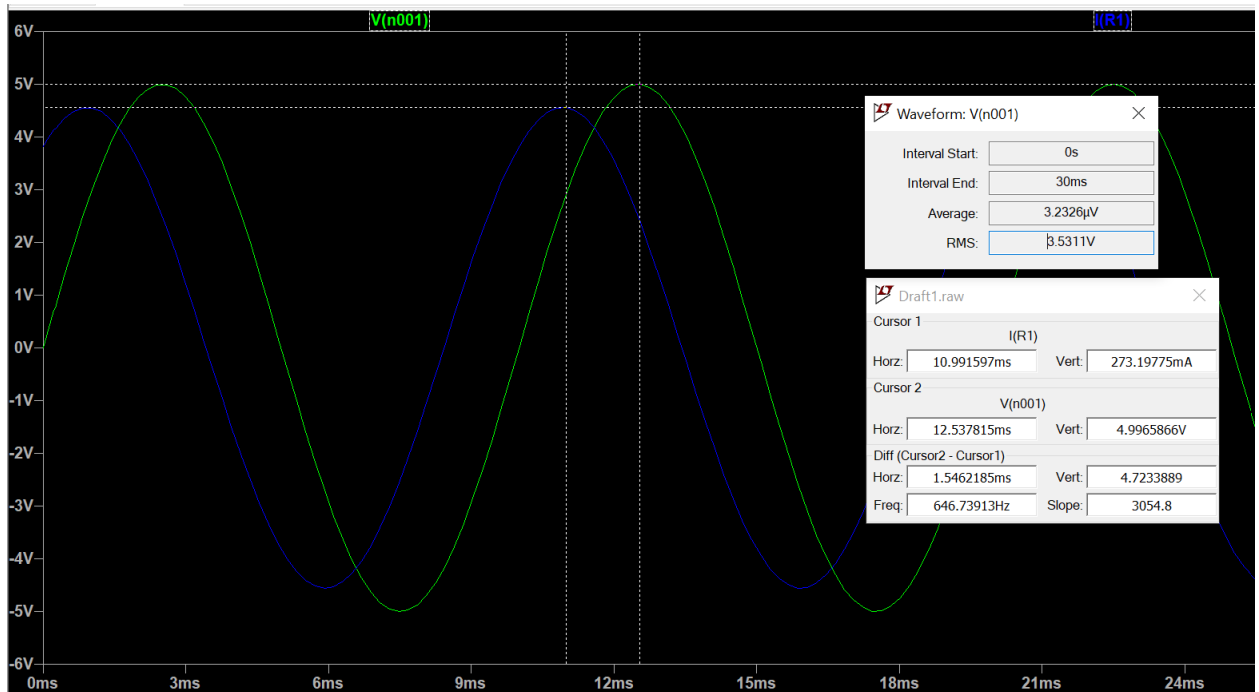


$$\text{Phase diff} = 1.579\text{ms} \times 360 \times 100 = 56.88$$

For VL

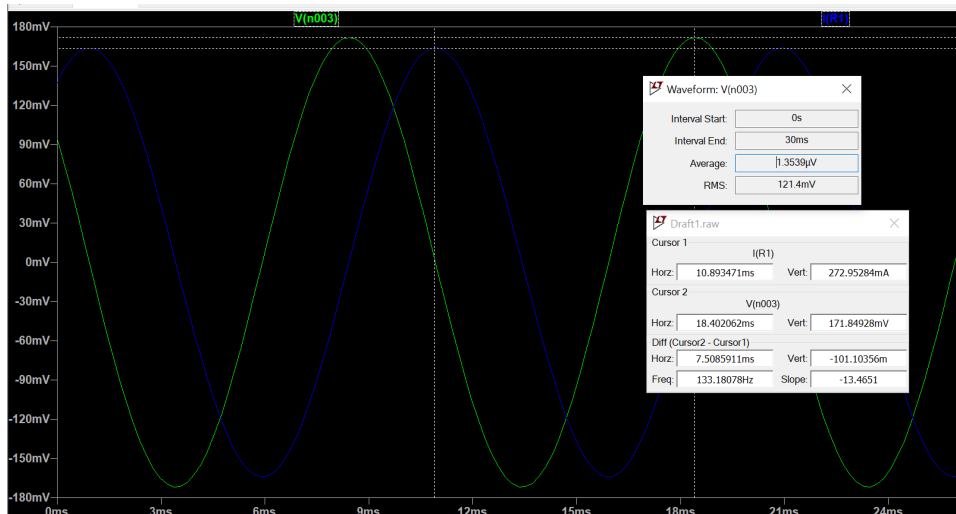


$$\text{Phase diff} = 7.508\text{ms} * 360 * 100 = 270.288$$

For Vc

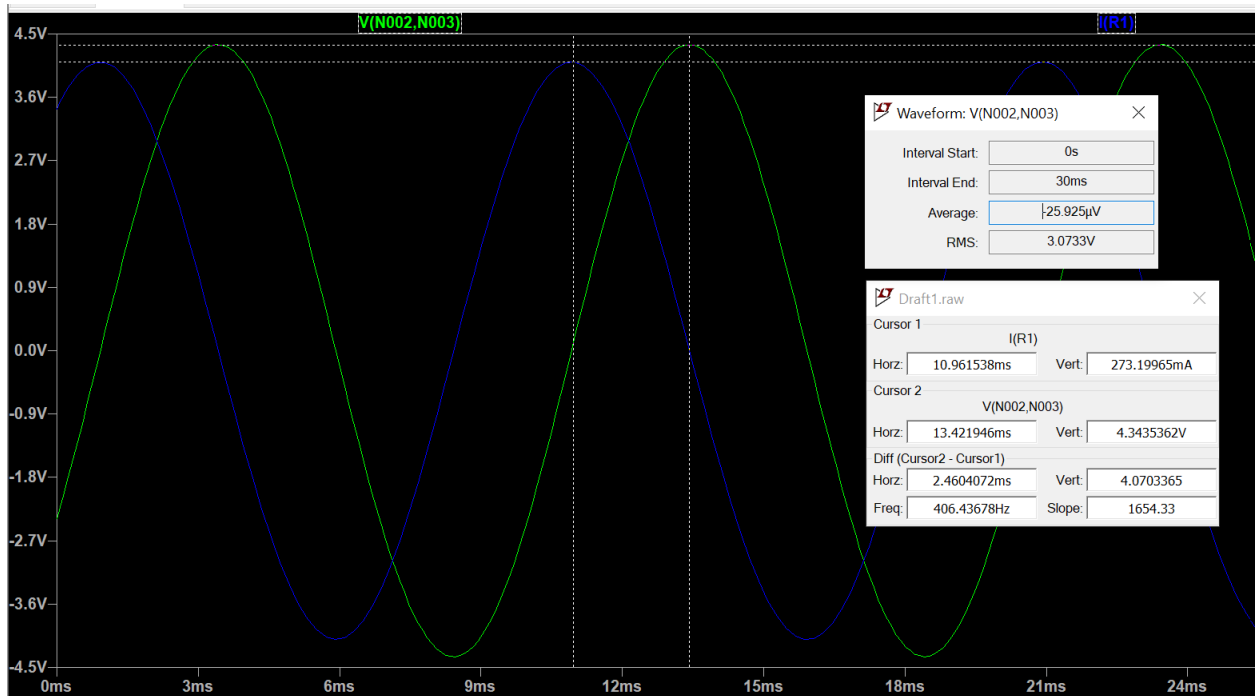

$$\text{Phase diff} = 2.4608\text{ms} * 360 * 100 = 91.2$$


For Vr

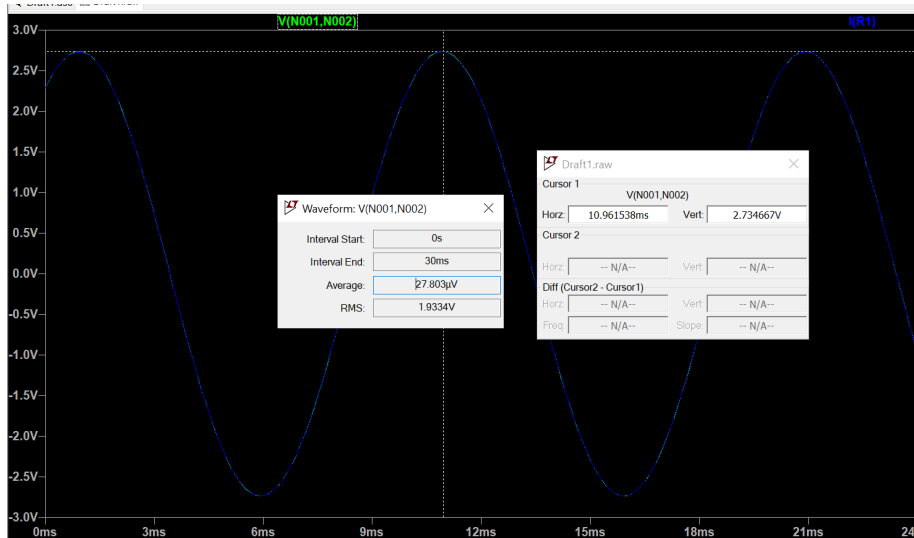

$$\text{Phase diff} = 0$$


2) For 500 Hz frequency:

For V

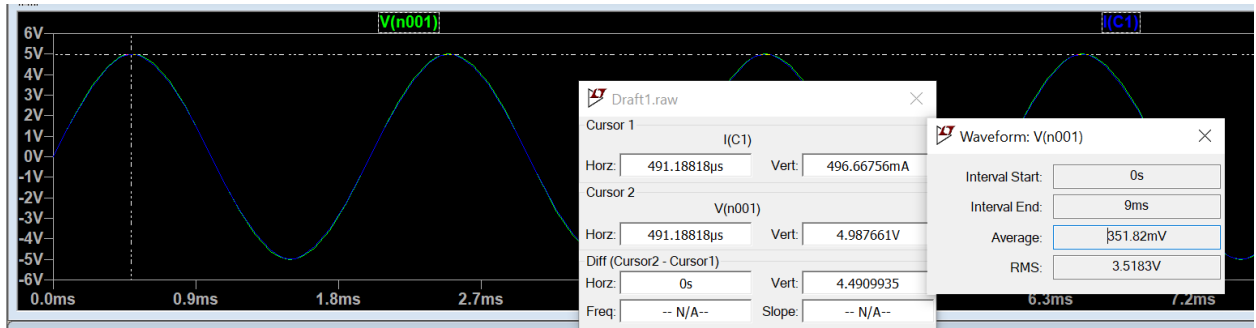


Phase diff = 0

For VL

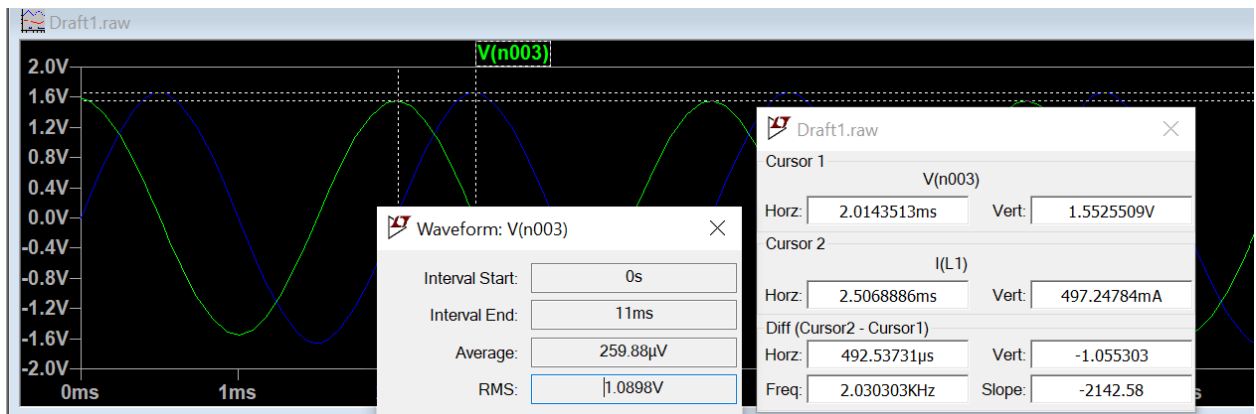


Phase diff = -88.56

For Vc

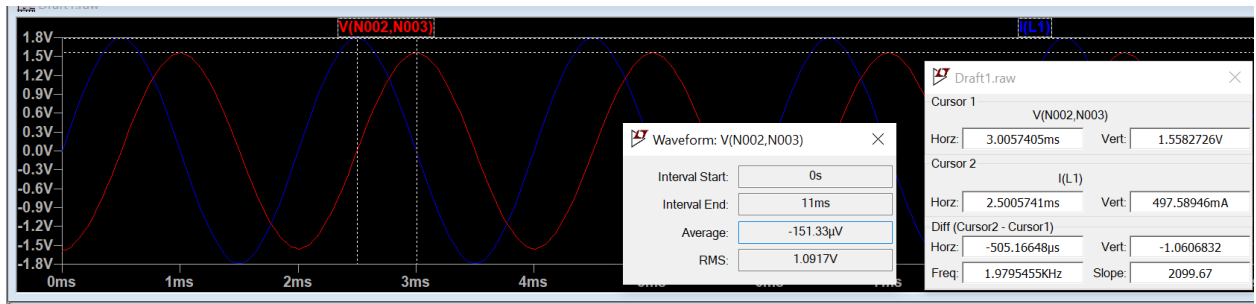

Phase diff = 90.9


For Vr

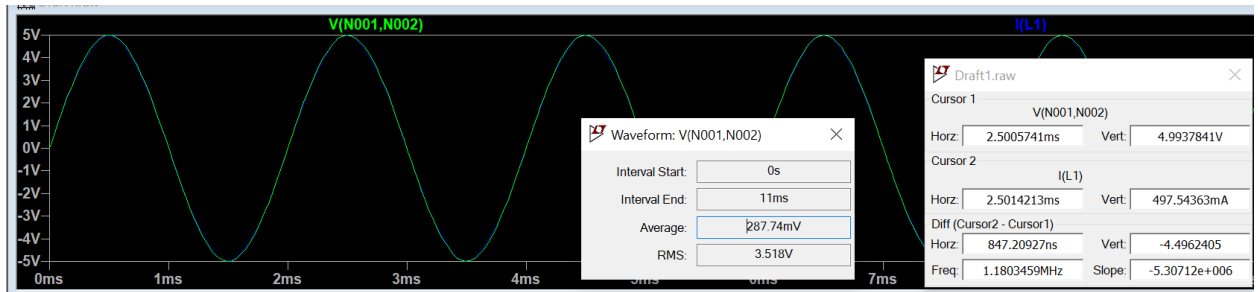

Phase diff = 0


3) For 700 Hz frequency:

For V

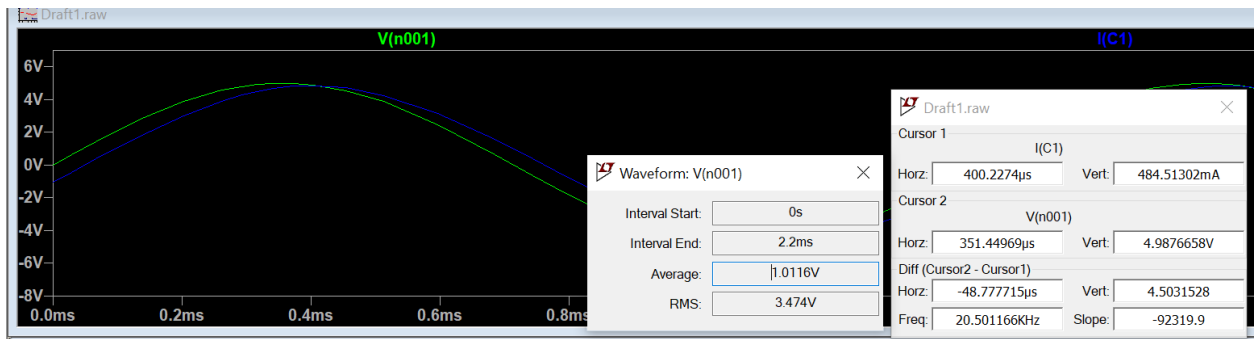


Phase diff = 12.1

For VL

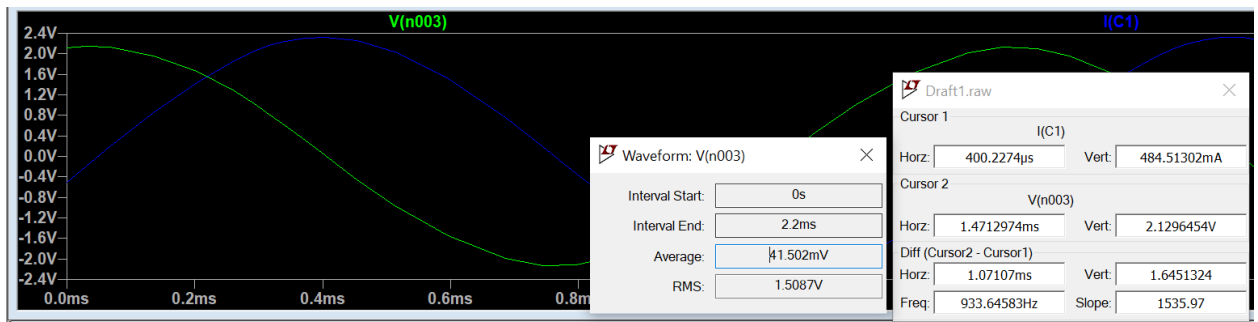


Phase diff = 269.6

For V_c

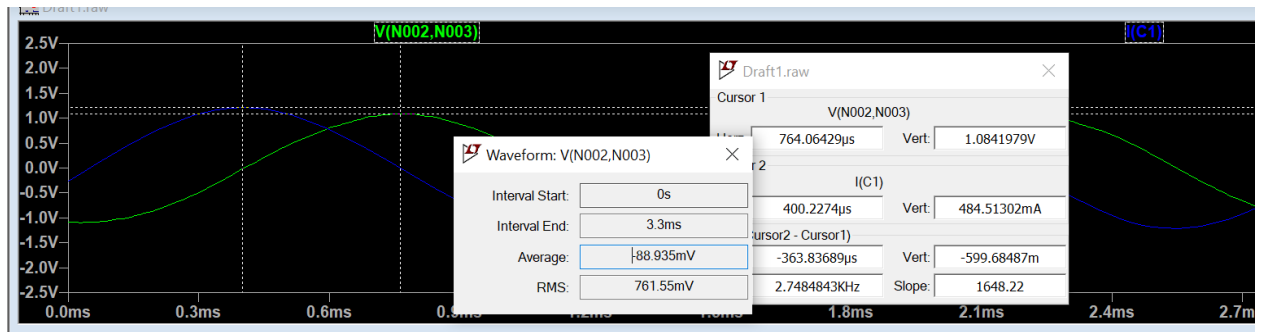

Phase diff = 91.4

For V_r

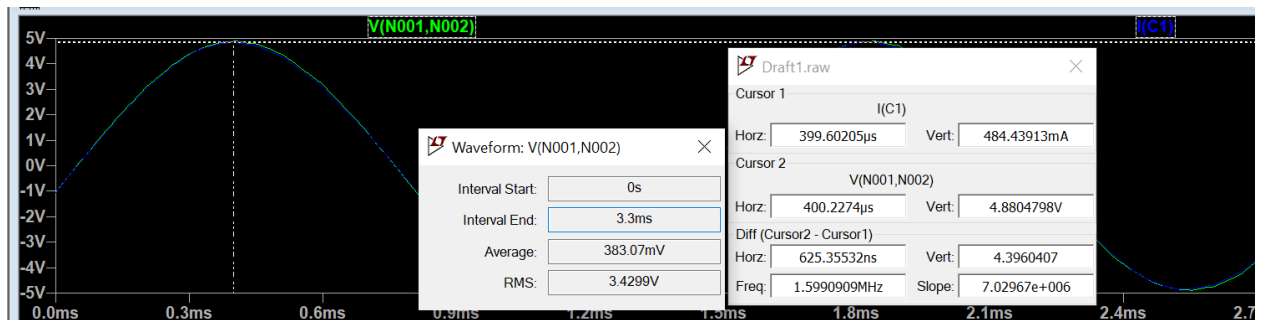

Phase diff = 0

Theoretical calculations(for practical inductor) :

1) For $f = 100\text{Hz}$

Practical for Inductor.

$$\text{for } \omega = 100 \text{ Hz.}$$

$$\omega = 628$$

$$R = 10 \Omega, L = 10^{-3} \text{ H}, C = 10^{-4} \text{ F}$$

$$X = 12.5 \Omega.$$

$$Z = (R + X) + j(\omega L - \frac{1}{\omega C})$$

$$X_L = 12.5 + j(0.628) \Omega.$$

$$= 12.51 \angle 2.876^\circ \Omega.$$

$$X_C = \frac{-j}{\omega C} = -j \left(\frac{10^4}{628} \right)$$

$$= -j(15.92) \Omega$$

$$Z = R + X_L + X_C$$

$$= 22.5 - j(15.29) \Omega.$$

$$Z = 27.2 \angle -34.2^\circ.$$

$$I = \frac{V}{Z} = \frac{5}{27.2} \angle 0^\circ$$

$$I_{rms} = \frac{0.183}{\sqrt{2}} \angle 34.2^\circ$$

$$= 0.13 \angle 34.2^\circ$$

$$V_L = I \cdot X_L$$

$$= 0.183 \times 15.51 \angle 2.876^\circ$$

$$= 2.88 \angle 2.87^\circ \text{ V}$$

$$V_{L,rms} = \frac{2.88}{\sqrt{2}} \angle 2.87^\circ \text{ V}$$

$$= 1.618 \angle 2.87^\circ \text{ V}$$

$$V_C = I \cdot X_C$$

$$= 0.183 \times (15.92) \angle -90^\circ$$

$$= 2.91 \angle -90^\circ$$

$$V_{C,rms} = 2.06 \angle -90^\circ$$

$$V_R = I \cdot R$$

$$= 1.83 \angle 34.2^\circ$$

$$V_{R,rms} = \frac{1.83}{\sqrt{2}} \angle 34.2^\circ$$

$$= 1.30 \angle 34.2^\circ$$

2) For $f = 500\text{Hz}$

$$f = 500\text{Hz}$$
$$\omega = 5 \times 628 = 3140$$
$$R = 10, L = 10^{-3}\text{H}, R = 12.5\Omega,$$
$$C = 10^{-4}\text{F}$$

$$X_L = R + j\omega L = 12.5 + j(3140)(10^{-3})$$
$$= 12.5 + j(3.14)\Omega$$
$$= 12.88 \angle 14.1^\circ \Omega$$

$$X_C = \frac{-j}{\omega C} = -j\left(\frac{10^4}{3140}\right)$$
$$= -j(3.18)$$

$$Z = R + X_L + X_C$$

$$= 22.5 + j(3.14 - 3.18)$$
$$= 22.5 - j(0.04)$$
$$= 22.5 \angle 0.1^\circ$$
$$\approx 22.5 \angle 0^\circ \Omega$$

$$I = \frac{V}{Z} = \frac{5 \angle 0^\circ}{22.5 \angle 0^\circ} = 0.22 \angle 0^\circ \text{A}$$

$$I_{\text{RMS}} = \frac{0.22 \angle 0^\circ}{\sqrt{2}} = 0.157 \angle 0^\circ \text{A}$$

$$V_L = I \cdot X_L = |I \cdot X_L| \angle 14.1^\circ$$

$$= (0.22)(12.88) \angle 14.1^\circ$$

$$= 2.83 \angle 14.1^\circ \text{ V}$$

$$V_{L_{\text{rms}}} = \frac{2.83}{\sqrt{2}} \angle 14.1^\circ$$

$$= 2 \angle 14.1^\circ \text{ V}$$

$$V_C = |I \cdot X_C| \angle -90^\circ$$

$$= (0.22)(3.18) \angle -90^\circ$$

$$= 0.7 \angle -90^\circ \text{ V}$$

$$V_{C_{\text{rms}}} = \frac{0.7}{\sqrt{2}} \angle -90^\circ \text{ V}$$


$$= 0.49 \angle -90^\circ \text{ V}$$

$$V_R = I \cdot R = 10 \times 0.222 \angle 0^\circ$$

$$= 2.22 \angle 0^\circ \text{ V}$$

$$V_{R_{\text{rms}}} = \frac{2.22}{\sqrt{2}} \angle 0^\circ \text{ V}$$

$$= 1.57 \angle 0^\circ \text{ V}$$

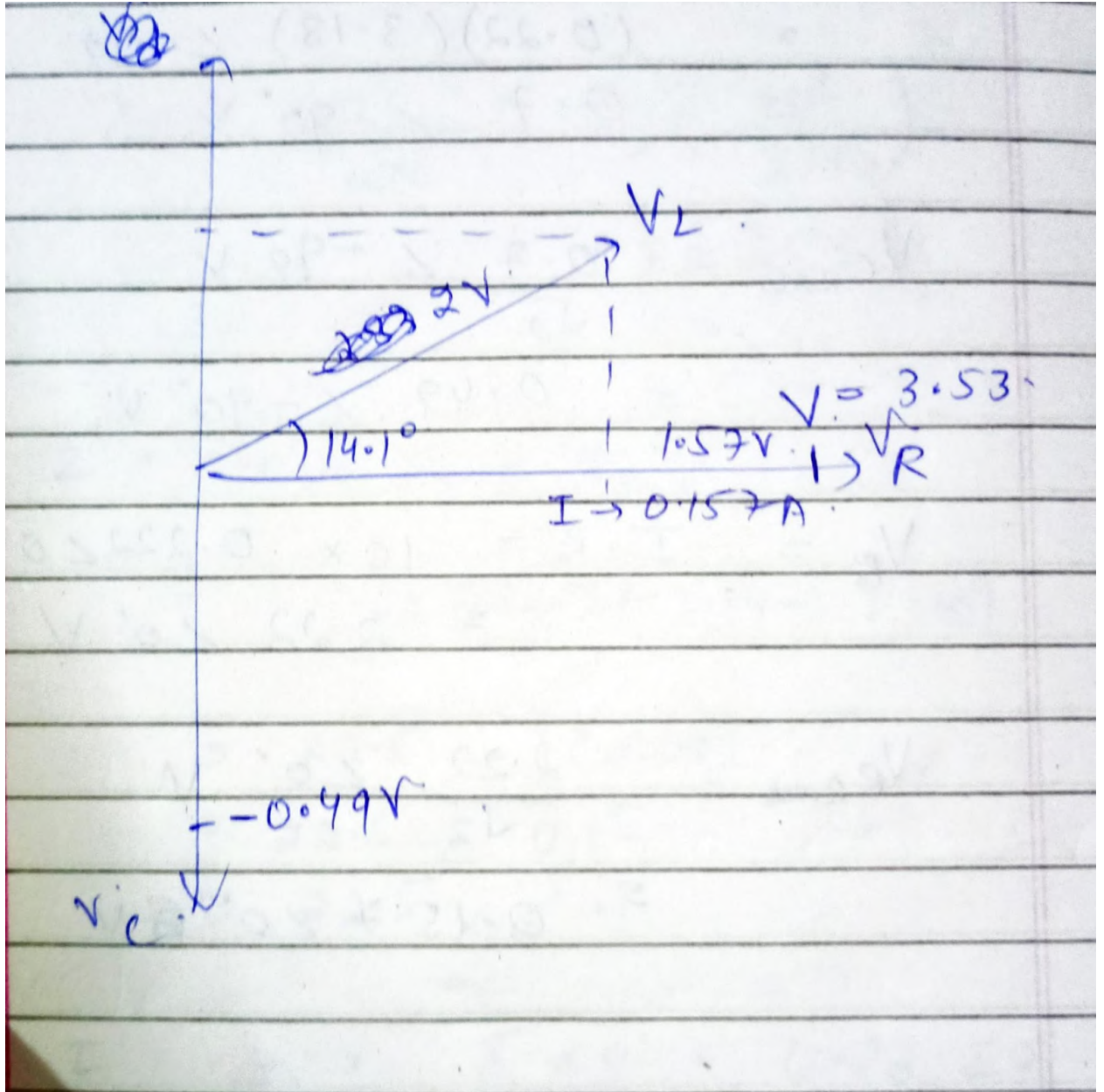

3) For $f = 700 \text{ Hz}$

$$\omega = 700 \text{ Hz}$$

$$\omega = 4396$$

$$R = 10 \Omega, L = 10^{-3} \text{ H}, R = 12.5 \Omega$$

$$C = 10^{-4} \text{ F}$$

$$X_L = j\omega L + R = 12.5 + j(4.396)$$

$$= 13.25 \angle 19.37^\circ$$

$$X_C = \frac{-j}{\omega C} = -j \left(\frac{10^4}{4396} \right)$$

$$= -j(2.274) \Omega$$

$$Z = 10 + 12.5 + j(4.396 - 2.274)$$

$$= 22.5 + j(2.12)$$

$$= 22.6 \angle 5.38^\circ$$

$$\phi = \angle 5.38^\circ$$

$$I = \frac{V}{Z} = \frac{5 \angle 0^\circ}{22.6 \angle 5.38^\circ}$$

$$= \cancel{22.2} 0.221 \angle -5.38^\circ$$

$$I_{RMS} = \frac{0.221 \angle -5.38^\circ}{\sqrt{2}}$$

$$I_{rms} = 0.156 \angle -5.38^\circ \text{ A}$$

$$\begin{aligned} V_L &= |I \cdot X_L| \angle \tan^{-1} \left(\frac{\omega L}{R} \right) \\ &= (0.221)(13.25) \angle 19.37^\circ \\ &= 2.928 \angle 19.37^\circ \text{ V} \end{aligned}$$

$$\begin{aligned} V_{L_{rms}} &= \frac{2.928}{\sqrt{2}} \angle 19.37^\circ \\ &= 2.07 \angle 19.37^\circ \text{ V} \end{aligned}$$

$$\begin{aligned} V_C &= |I \cdot X_C| \angle -90^\circ \\ &= (0.221)(2.274) \angle -90^\circ \\ &= 0.502 \angle -90^\circ \end{aligned}$$

$$\begin{aligned} V_{C_{rms}} &= \frac{0.502}{\sqrt{2}} \angle -90^\circ \\ &= 0.355 \angle -90^\circ \end{aligned}$$


$$\begin{aligned} V_R &= I \cdot R = 0.221 \times 10 \angle -5.38^\circ \\ &= 2.21 \angle -5.38^\circ \text{ V} \end{aligned}$$

$$\begin{aligned} V_{R_{rms}} &= \frac{2.21}{\sqrt{2}} \angle -5.38^\circ \\ &= 1.56 \angle -5.38^\circ \text{ V} \end{aligned}$$

Practical observations(practical inductor):


1) For 100 Hz frequency:

For V

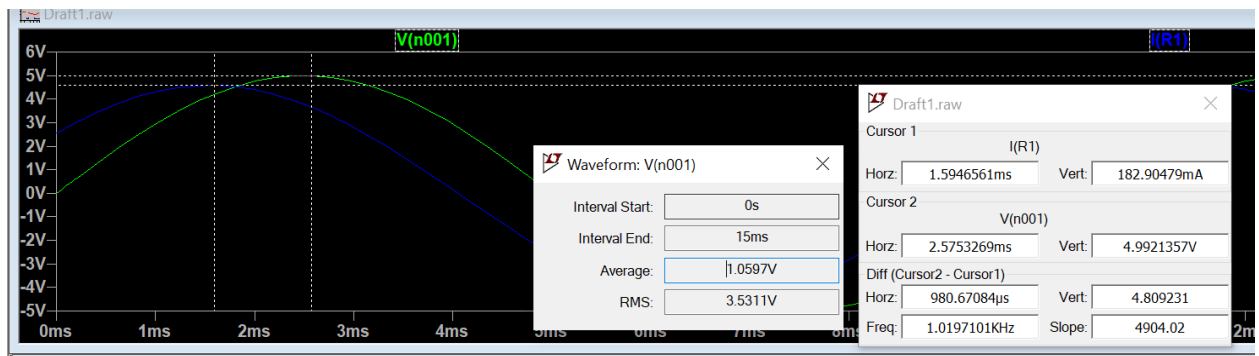


Phase diff = 35.2

For VL

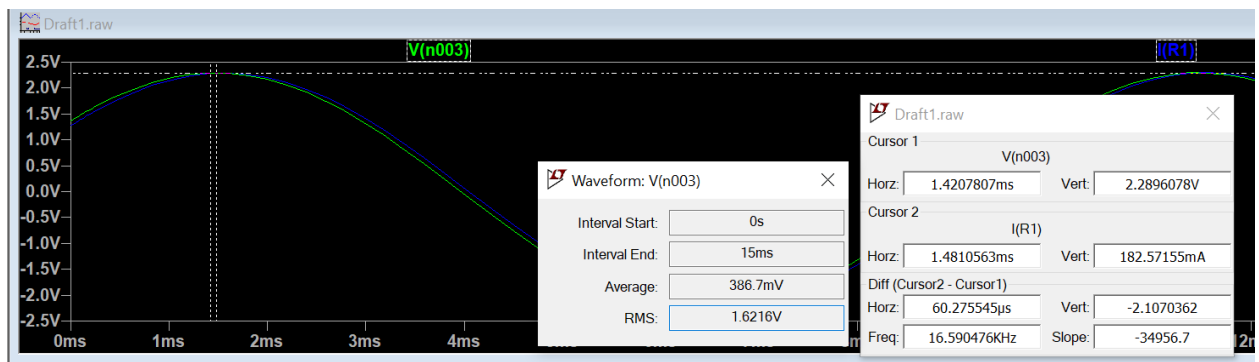


Phase diff = -2.16 or (360- 2.16)

For Vc

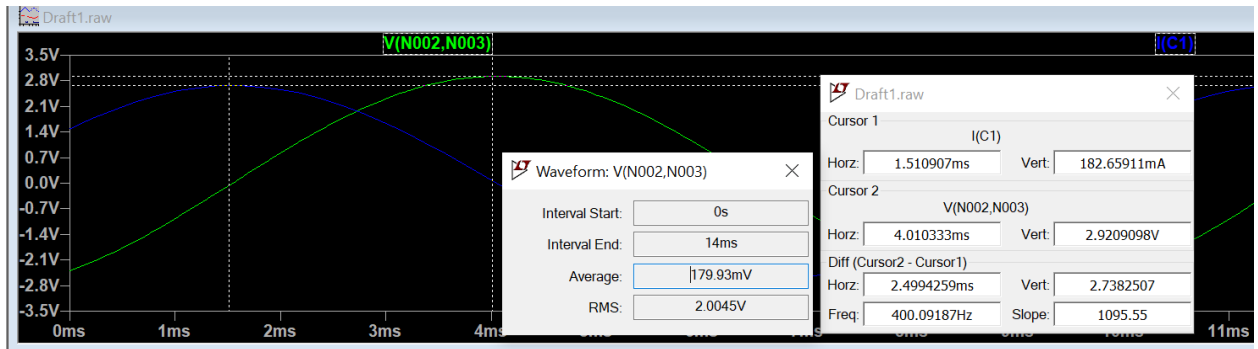

Phase diff = 89.64


For Vr

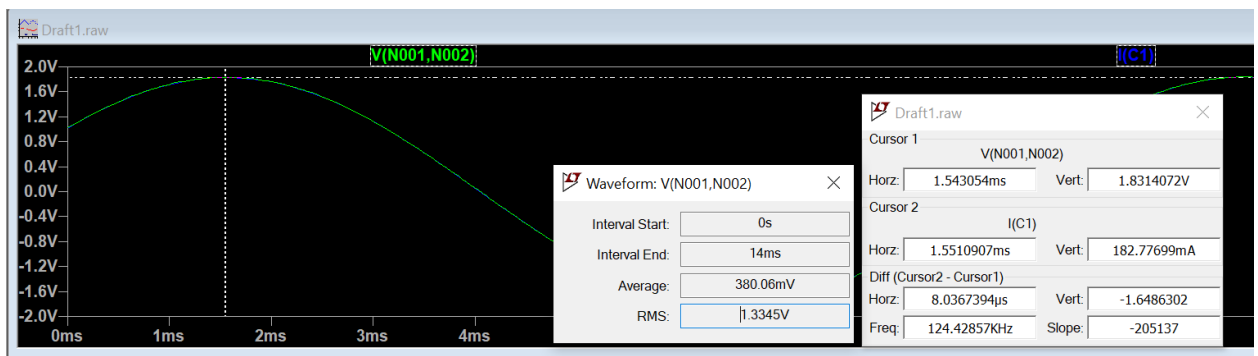

Phase diff = 0


2) For 500 Hz frequency:

For V

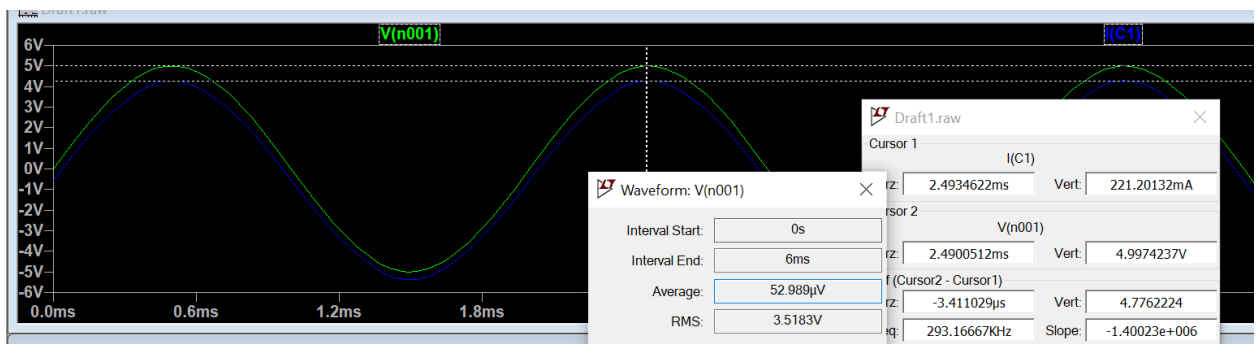


Phase diff = 0

For VL

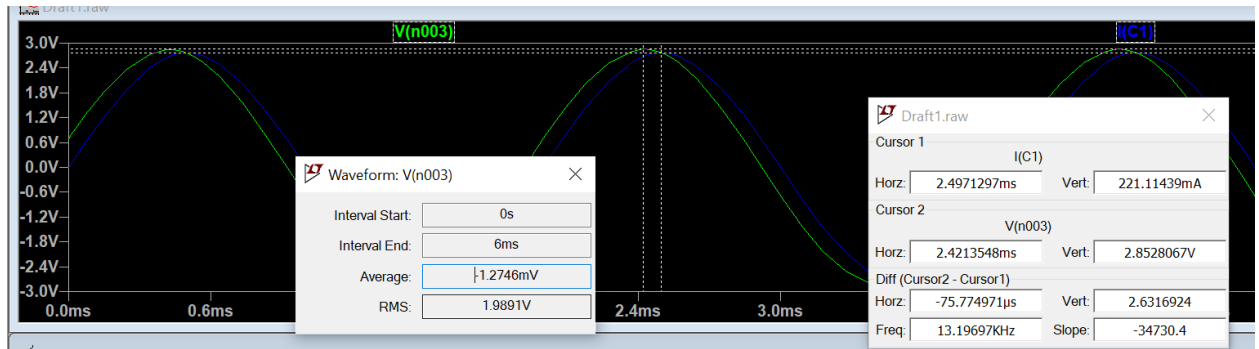


Phase diff = -13.5 or (360- 13.5)

For Vc

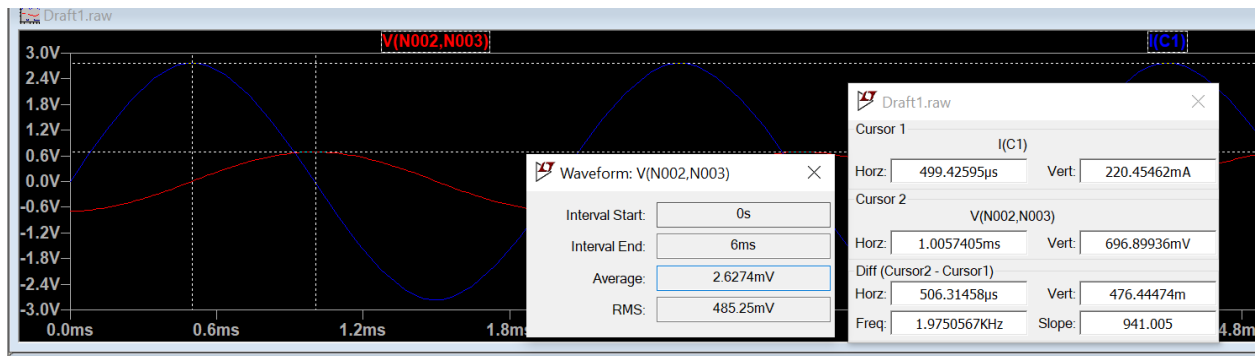

Phase diff = 91.1


For Vr

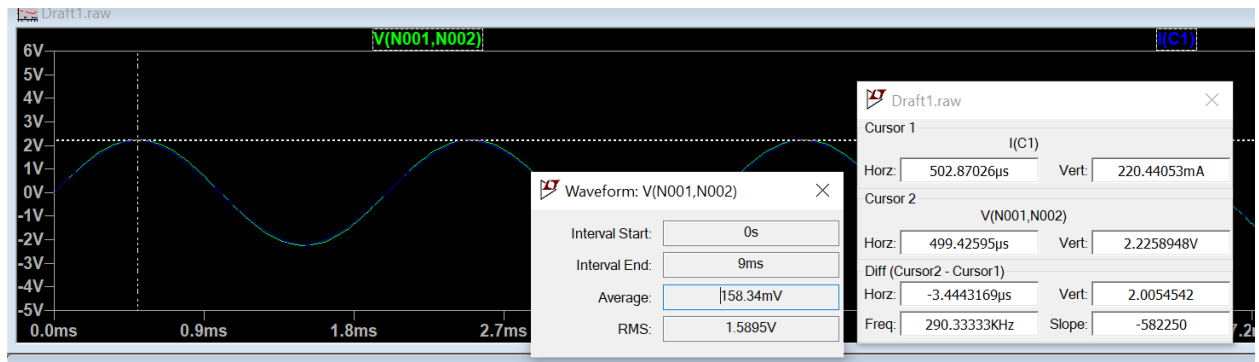

Phase diff = 0


3) For 700 Hz frequency:

For V

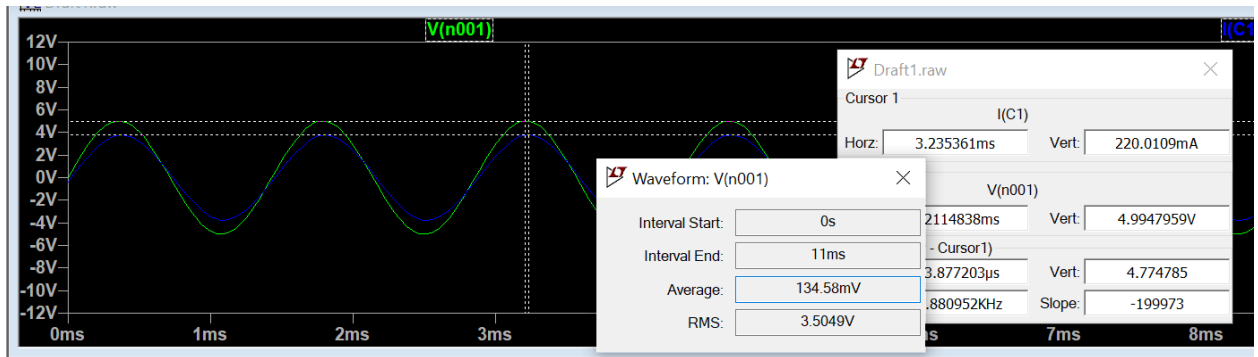


Phase diff = 5.8

For VL

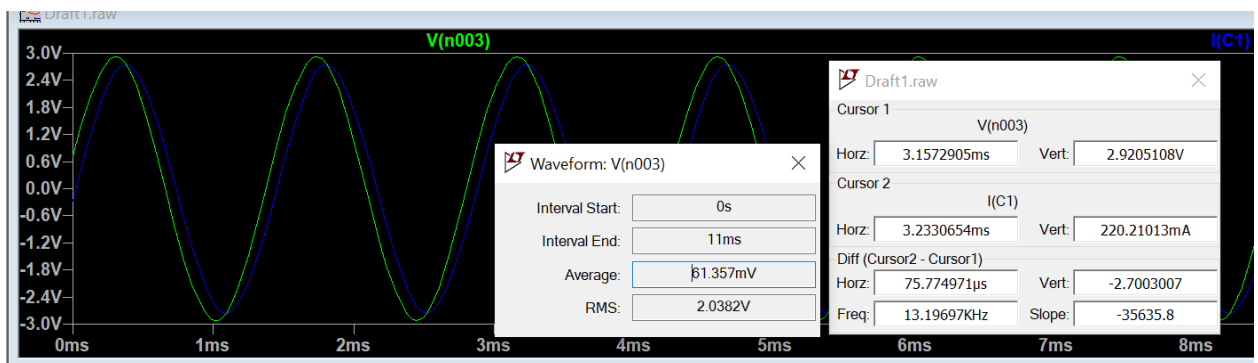


Phase diff = -19 or (360- 19)

For Vc

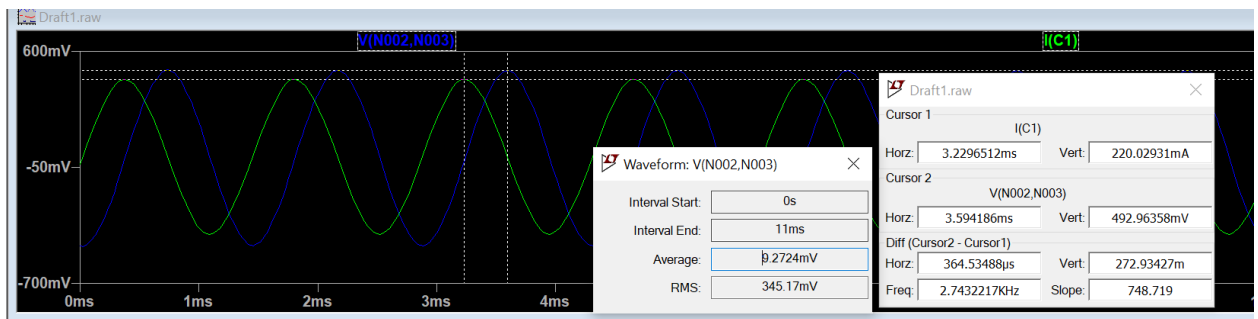

Phase diff = 90.8

For Vr

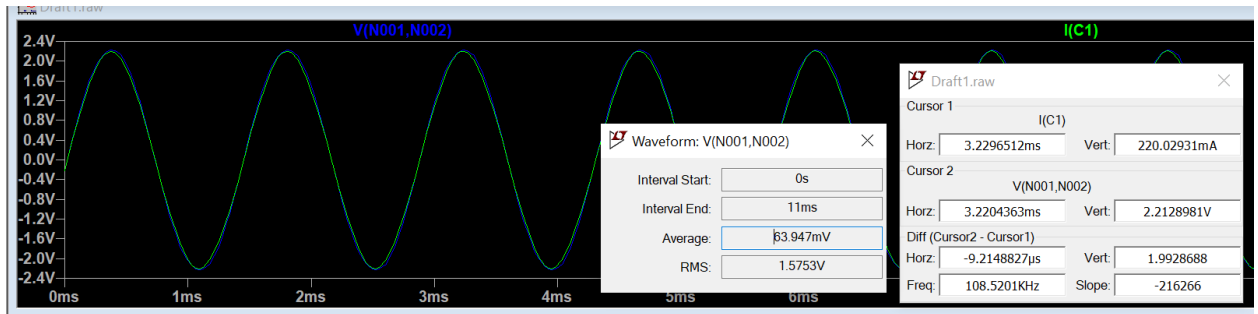

Phase diff = 0

Observations :

For ideal inductor

Input Freq	Mention phase (lag or lead) of the voltage waveforms w.r.t input current along with the rms values of the voltages.							
	Vr		VL		Vc		V	
	theoretical	practical	theoretical	practical	theoretical	practical	theoretical	practical
100Hz	1.93	1.933	.1212	0.1214	3.07	3.07	3.53	3.53
500Hz	3.53	3.518	1.11	1.09	1.12	1.09	3.53	3.53
700Hz	3.46	3.43	1.52	1.51	0.787	0.761	3.53	3.53

For practical inductor

Input Freq	Mention phase (lag or lead) of the voltage waveforms w.r.t input current along with the rms values of the voltages.							
	Vr		VL		Vc		V	
	theoretical	practical	theoretical	practical	theoretical	practical	theoretical	practical
100Hz	1.3	1.33	1.618	1.62	2.06	2	3.53	3.53

500Hz	1.57	1.589	2	2	0.49	.485	3.53	3.53
700Hz	1.56	1.57	2.07	2.03	0.355	.345	3.53	3.53

Applications :

1. RLC circuits have many applications as oscillator circuits.
 2. They are used in television sets and radio receivers for tuning purposes.
-