

ECE113|BASIC ELECTRONICS

Dr. S.S.Jamuar

Lab_7:

Student Name : Shivam Agarwal

Roll No. : 2020123

Date : 15/8/2021


AIM 1 :Simulate Half-Wave rectifier circuit, Diode Clipping circuit, and Diode Clamping circuit and observe the output waveforms on LTspice.

Components Used : voltage source ,resistor , Diode(1N914) ,capacitor , wires.


Software used : LTspice

Half Wave rectifier :

1) Circuit :

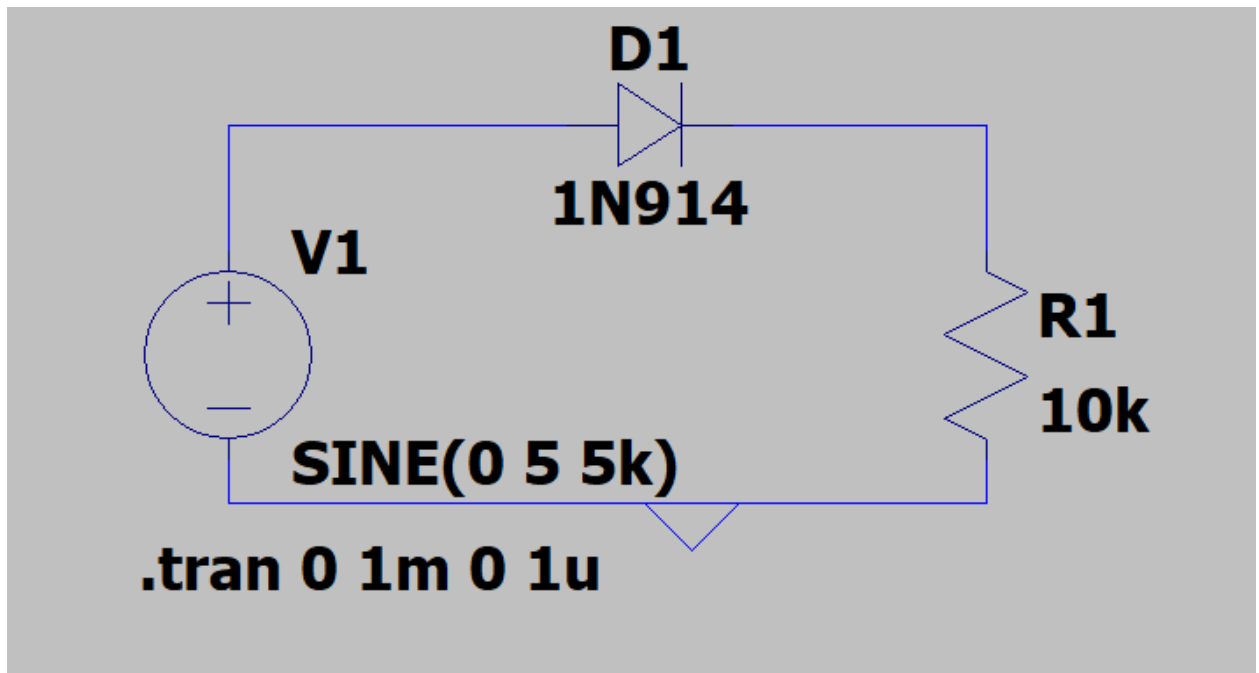

Waveform :

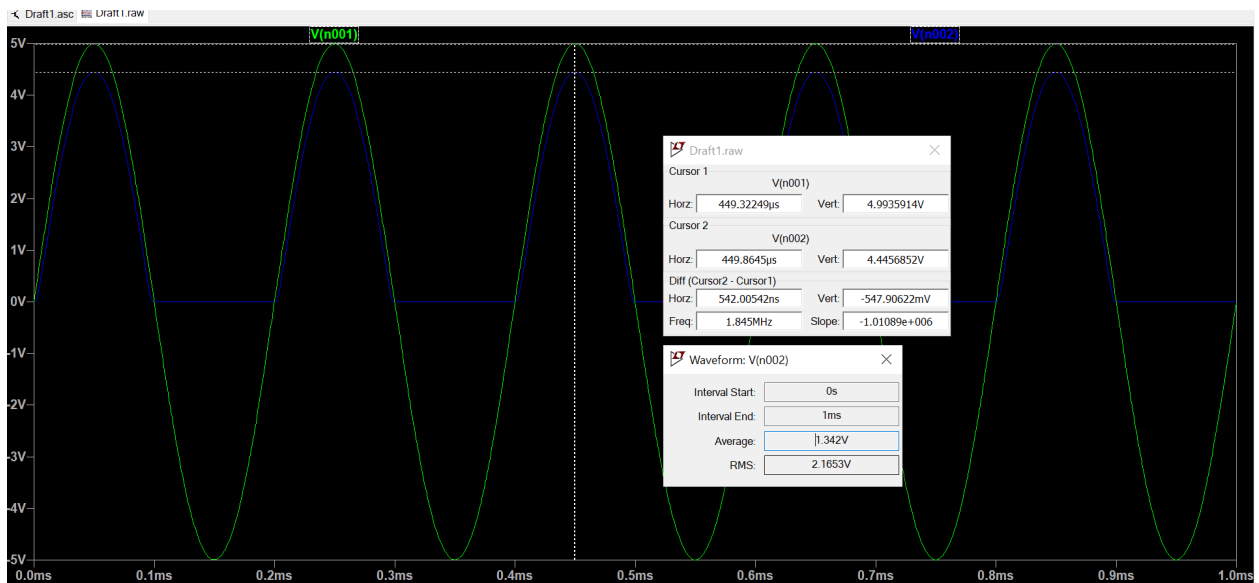

Peak value : 4.445V

Avg value: 1.342V


Theoretical calculations :

Average value :


$$\begin{aligned} DC &= \frac{V_m}{\pi} - \frac{V_F}{2} \\ &= \frac{5}{\pi} - \frac{0.55}{2} \\ &= 1.316 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{Peak value} &= V_m - V_F \\ &= 5 - 0.55 \\ &= 4.45 \text{ V} \end{aligned}$$

2) Circuit :

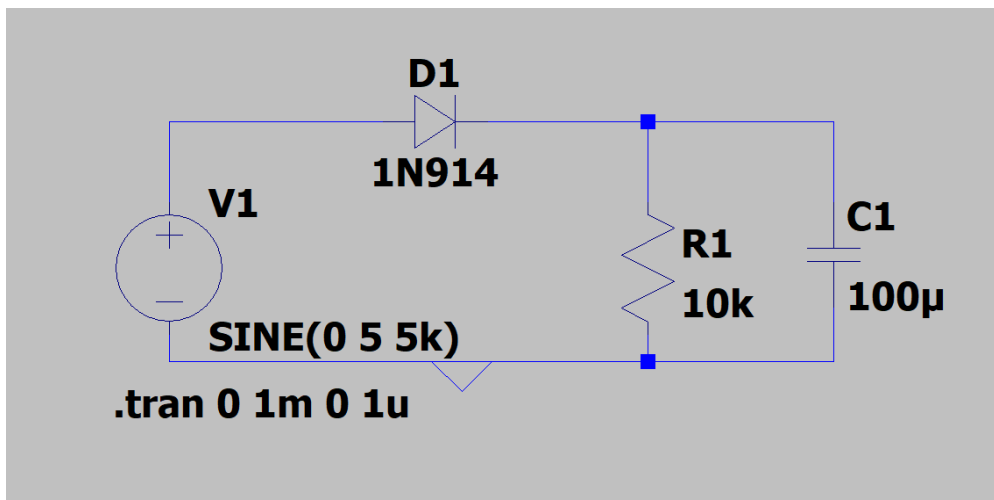


Waveform:

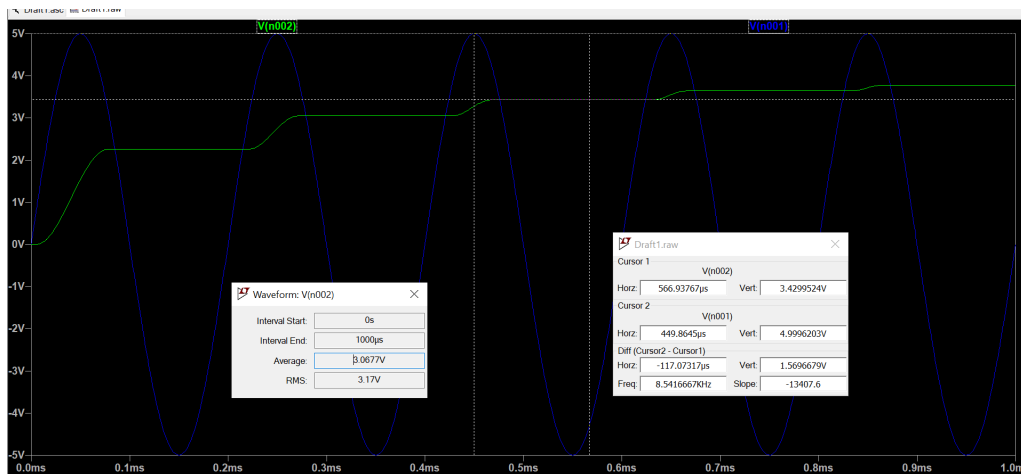


Peak value : 3.43V

Avg value: 3.067V

3) Circuit :

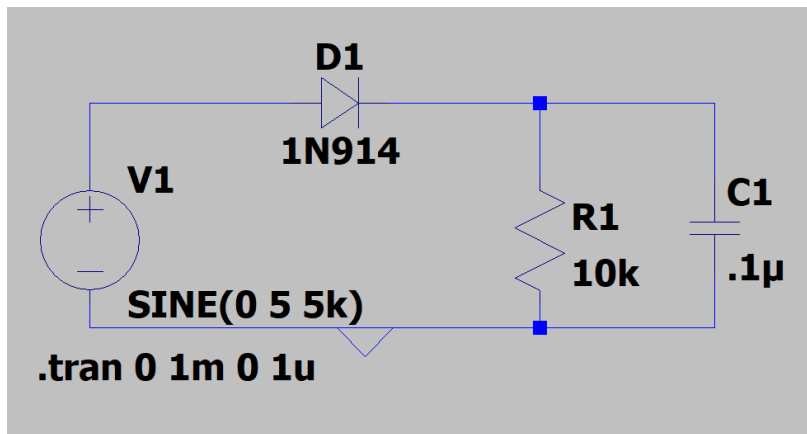


Waveform:

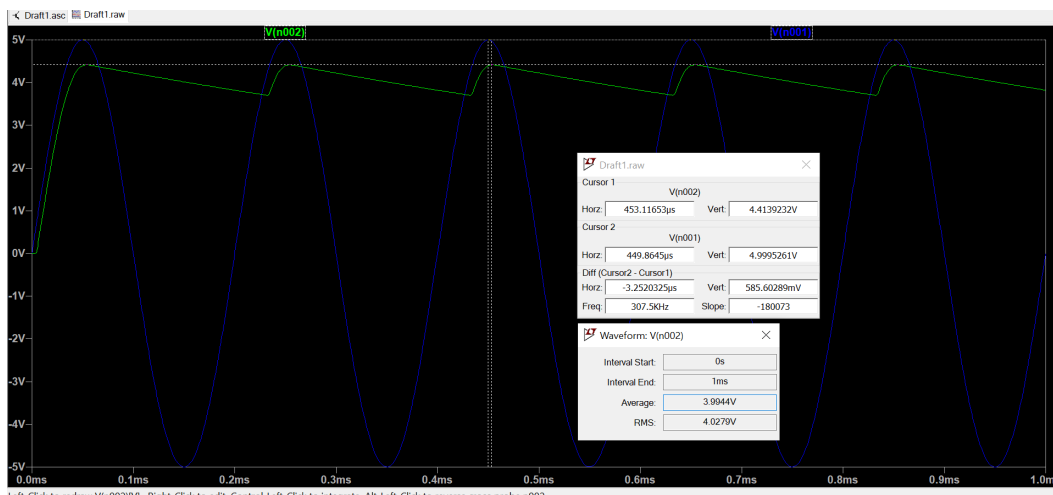


Peak value : 4.41V
Avg value: 4V

4) Circuit :

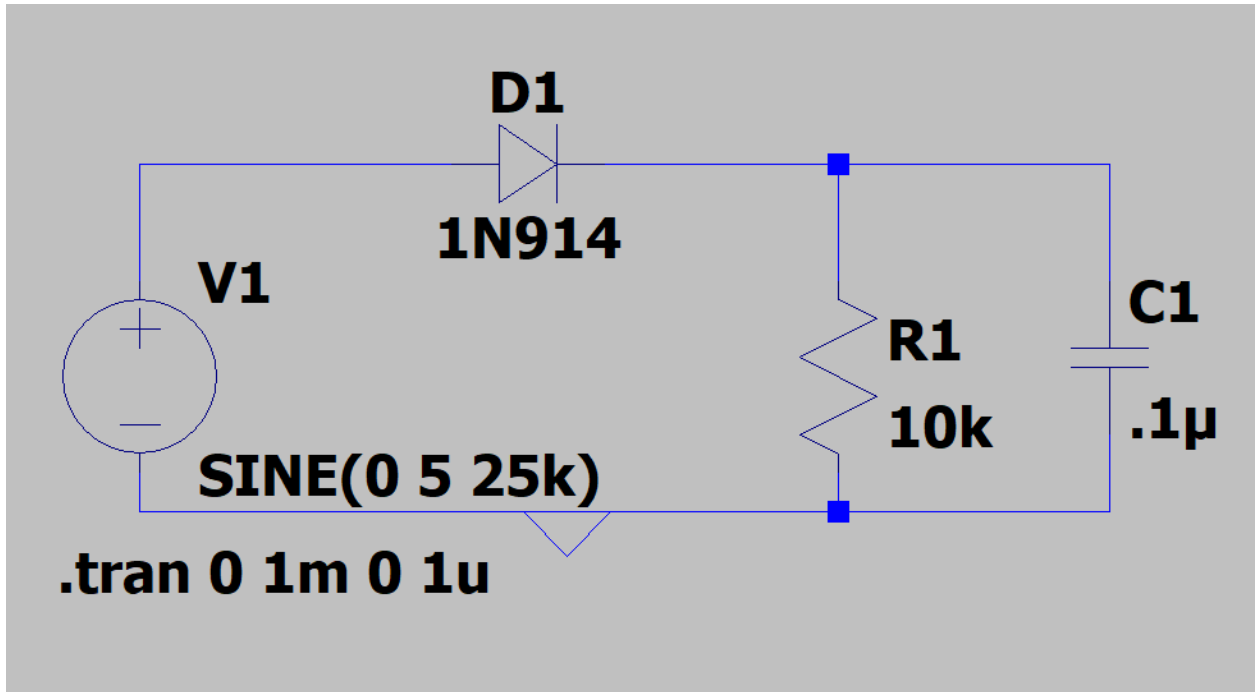


Waveform:

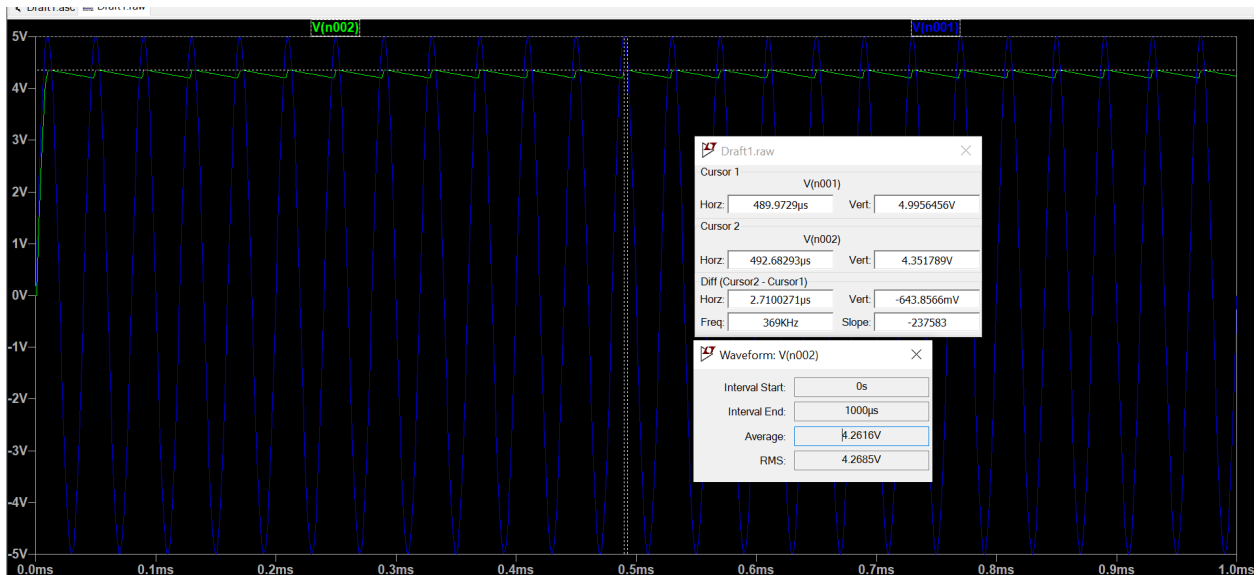


Peak value : 4.35V
Avg value: 4.26V

Diode Clipping Circuit :

1) Circuit :

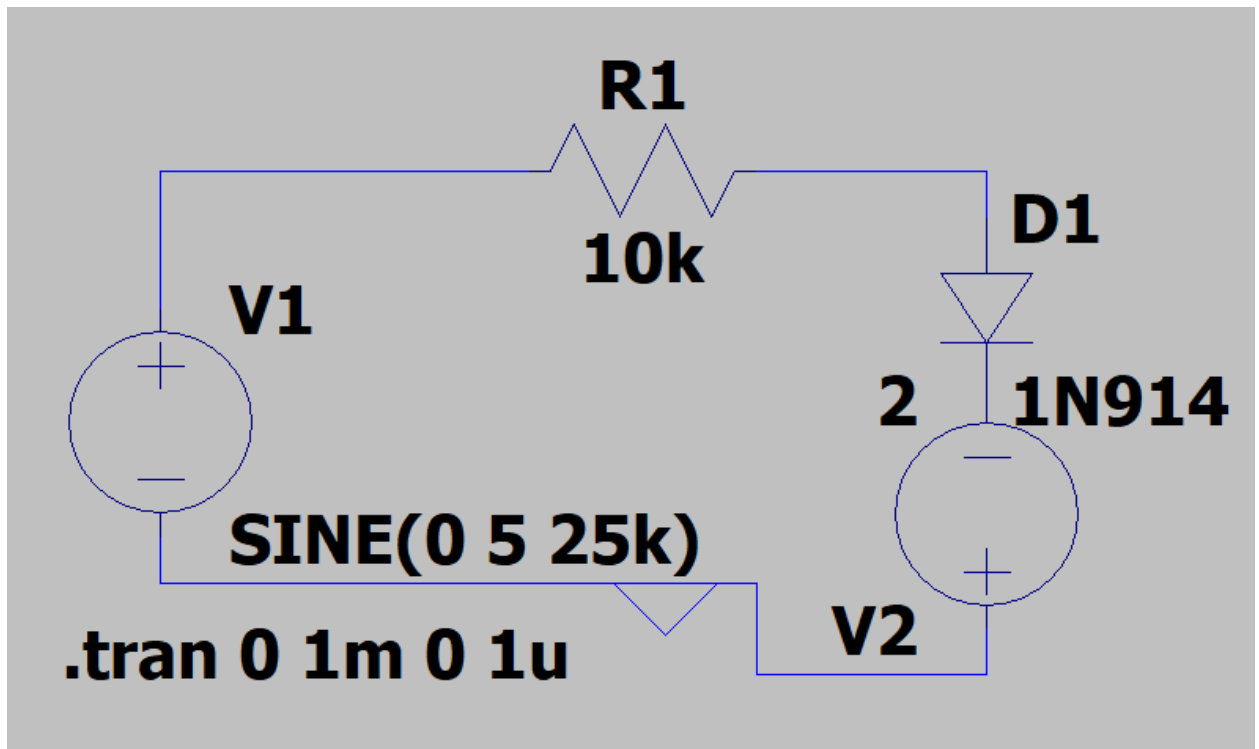


Waveform:

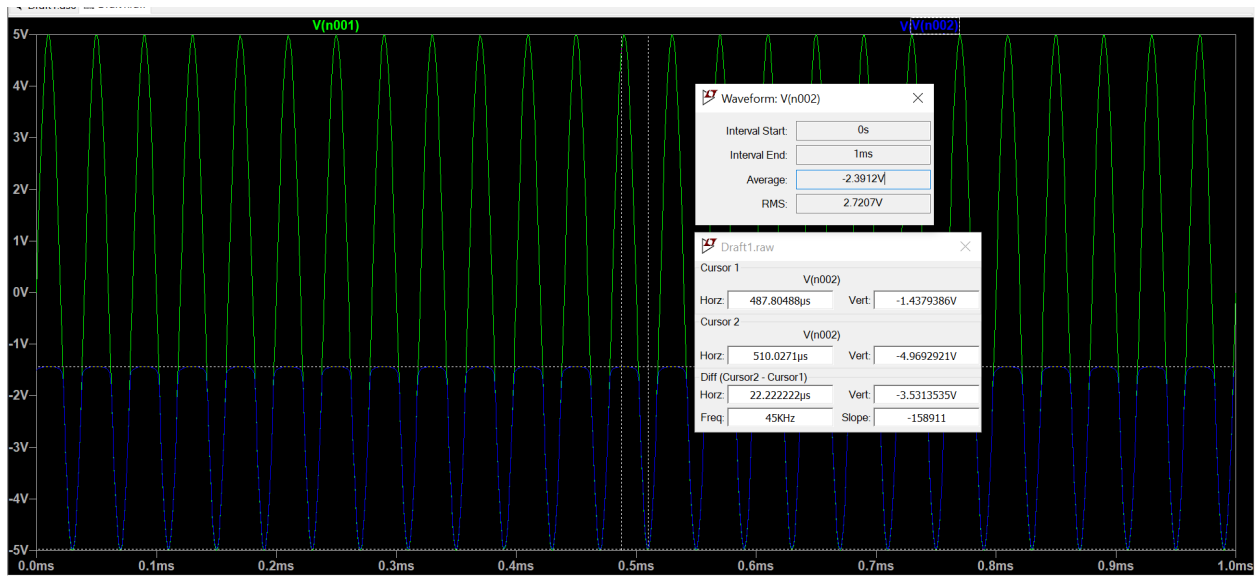


Peak value : -4.97V

Avg value: -2.39V

2) Circuit :

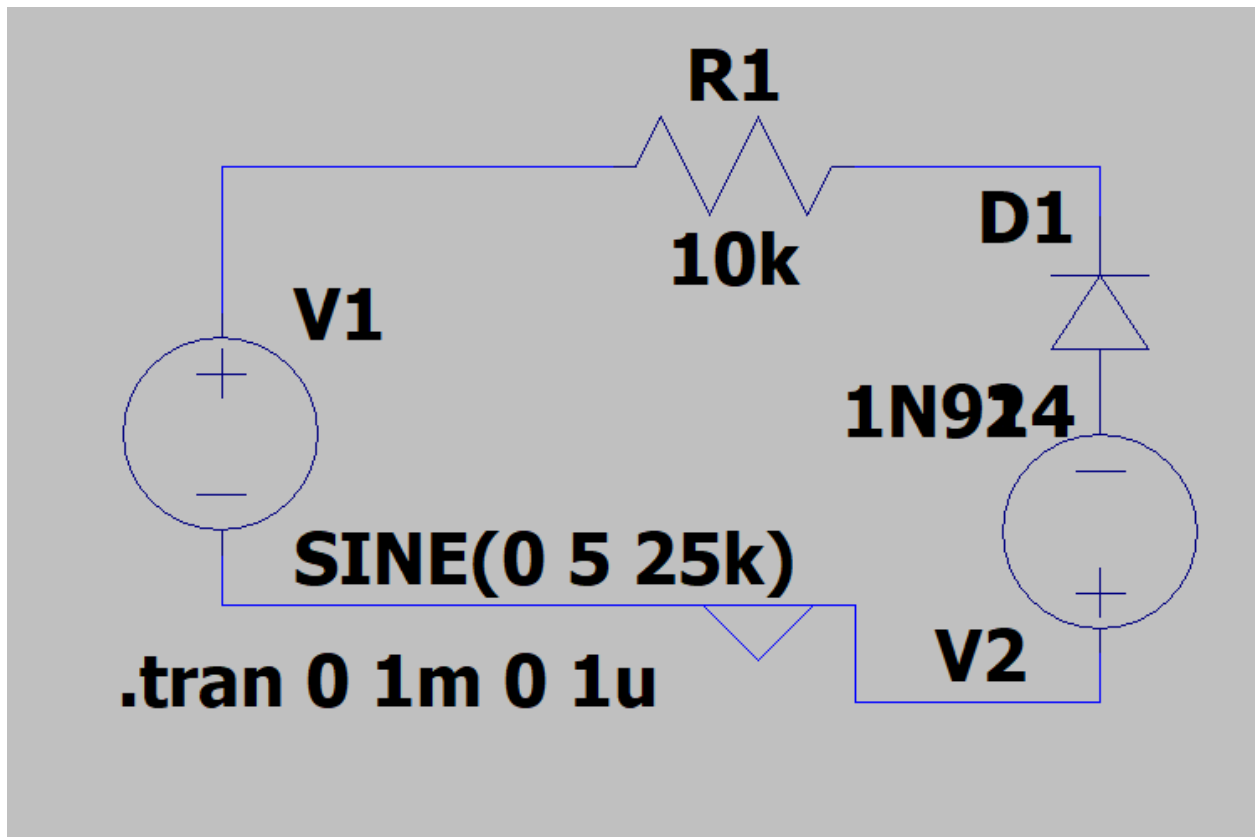

Waveform:

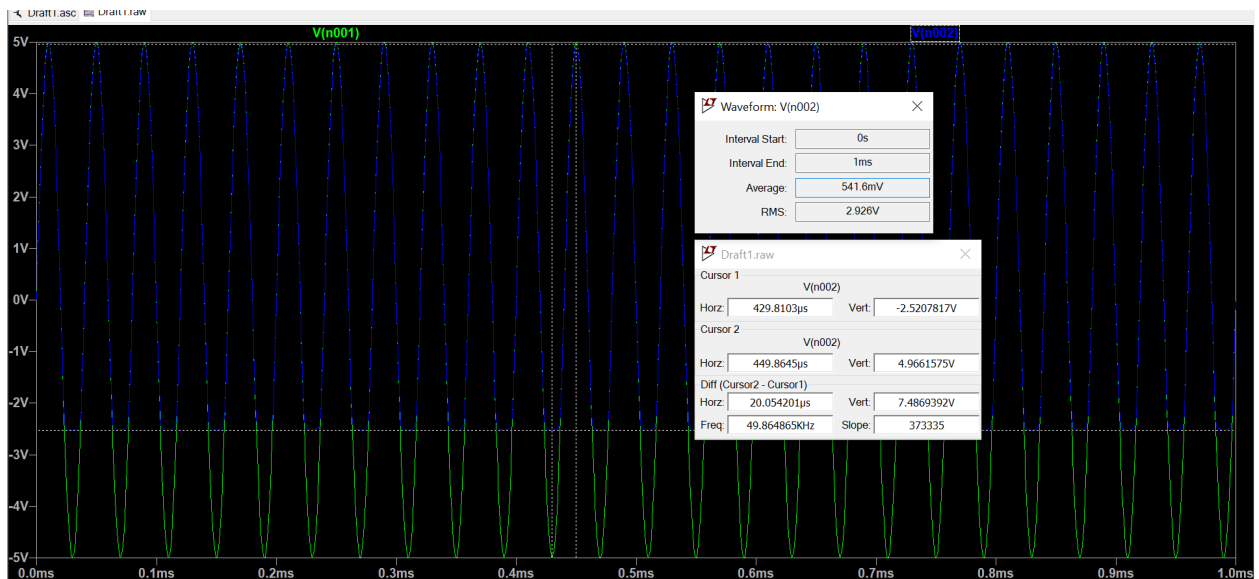


Peak value : 4.96V


Avg value: .541V

Diode Clamping Circuit :

1) Circuit :

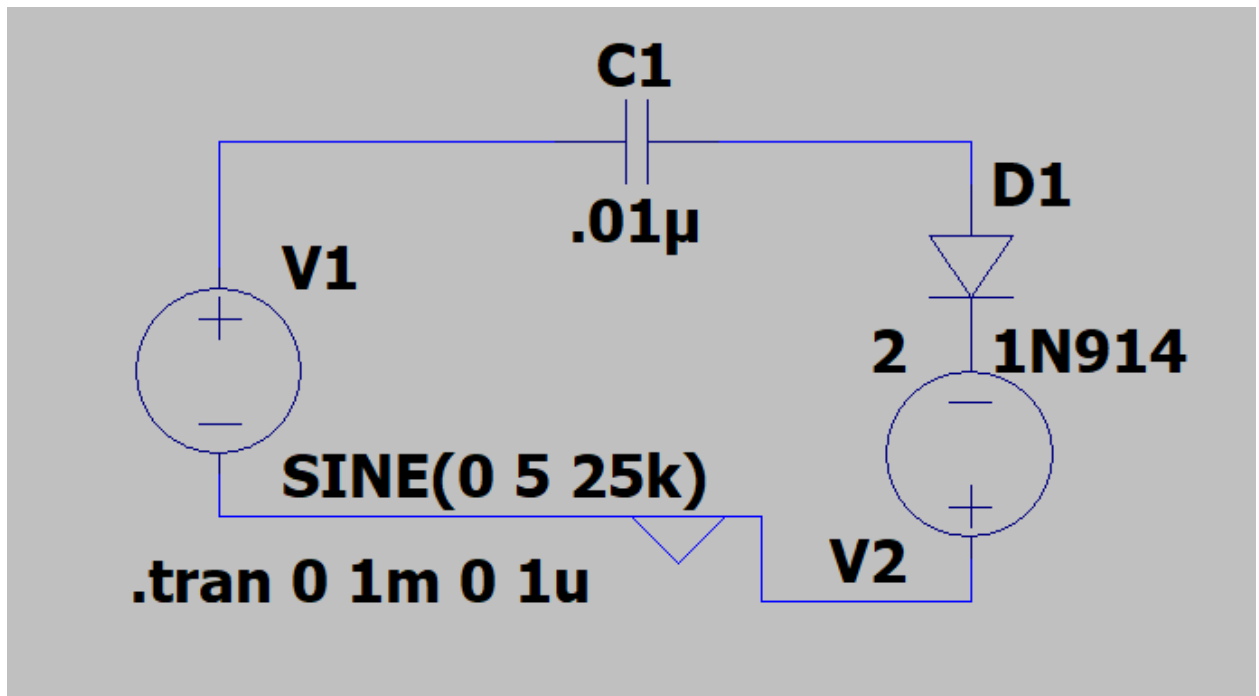


Waveform:

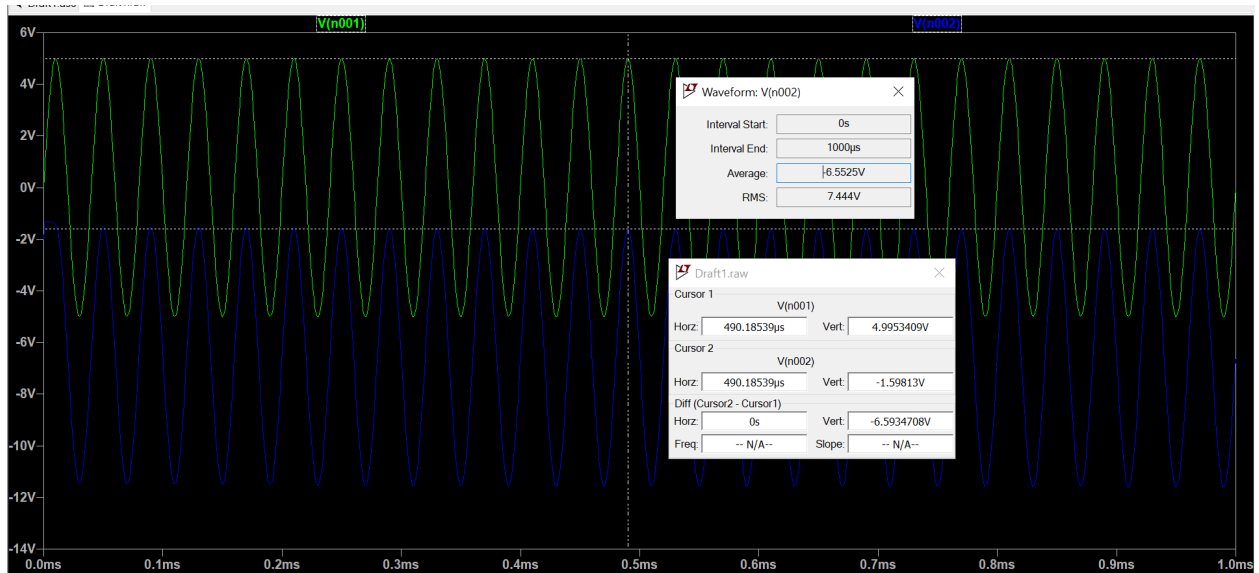


Peak value : -1.59V

Avg value: -6.55V

2) Circuit :

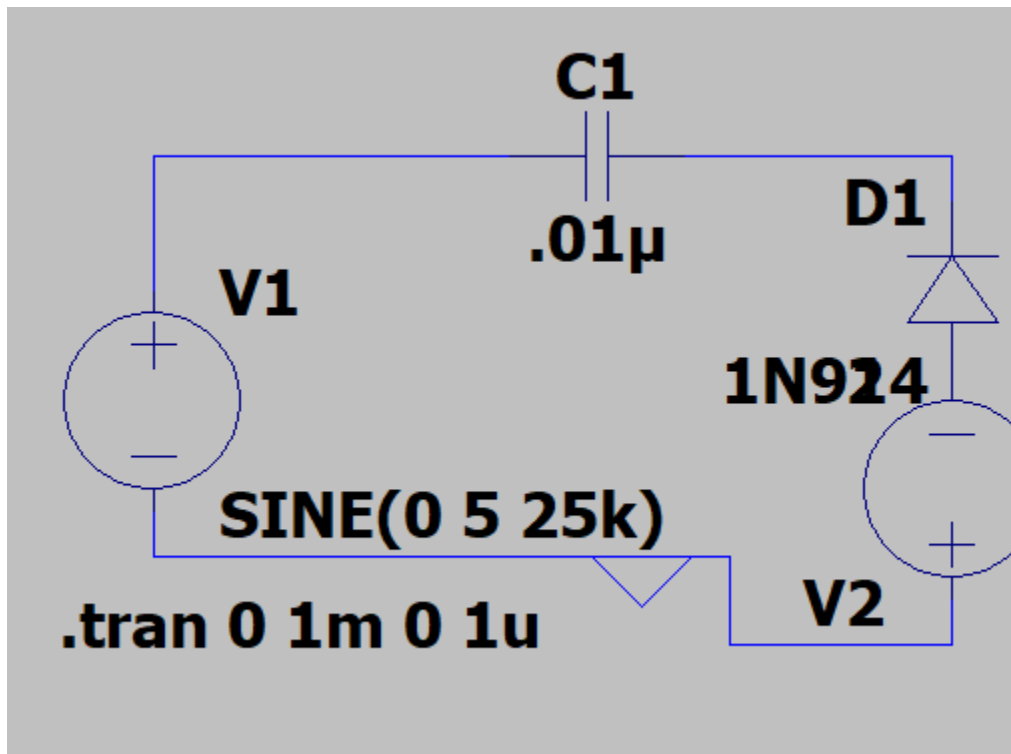


Waveform:

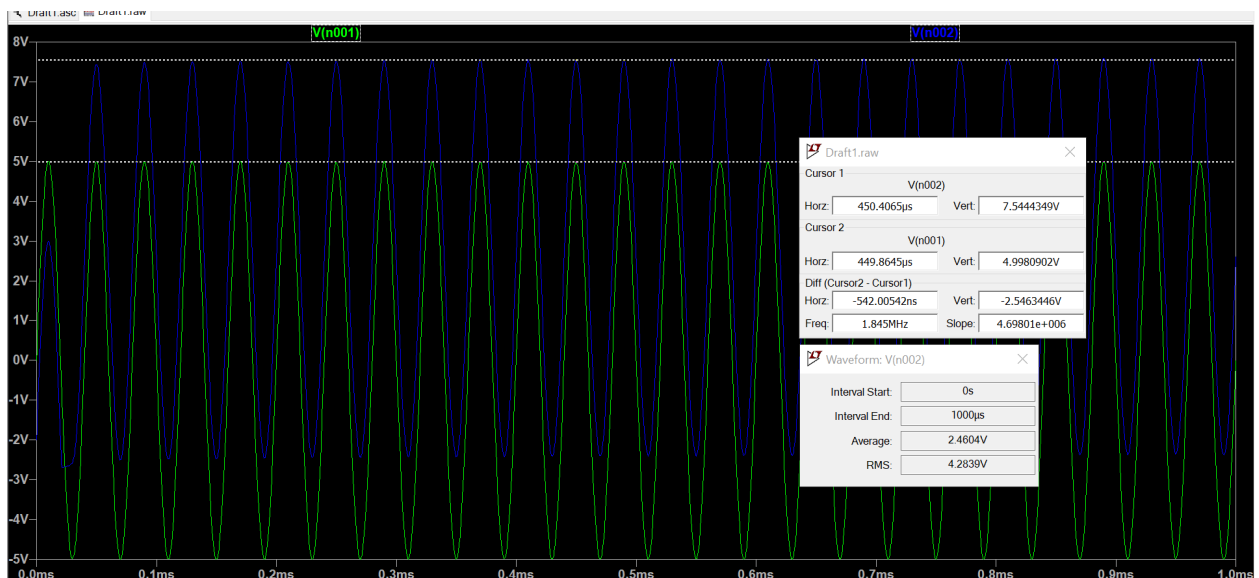


Peak value : 7.54V

Avg value: 2.46V

3) Circuit :

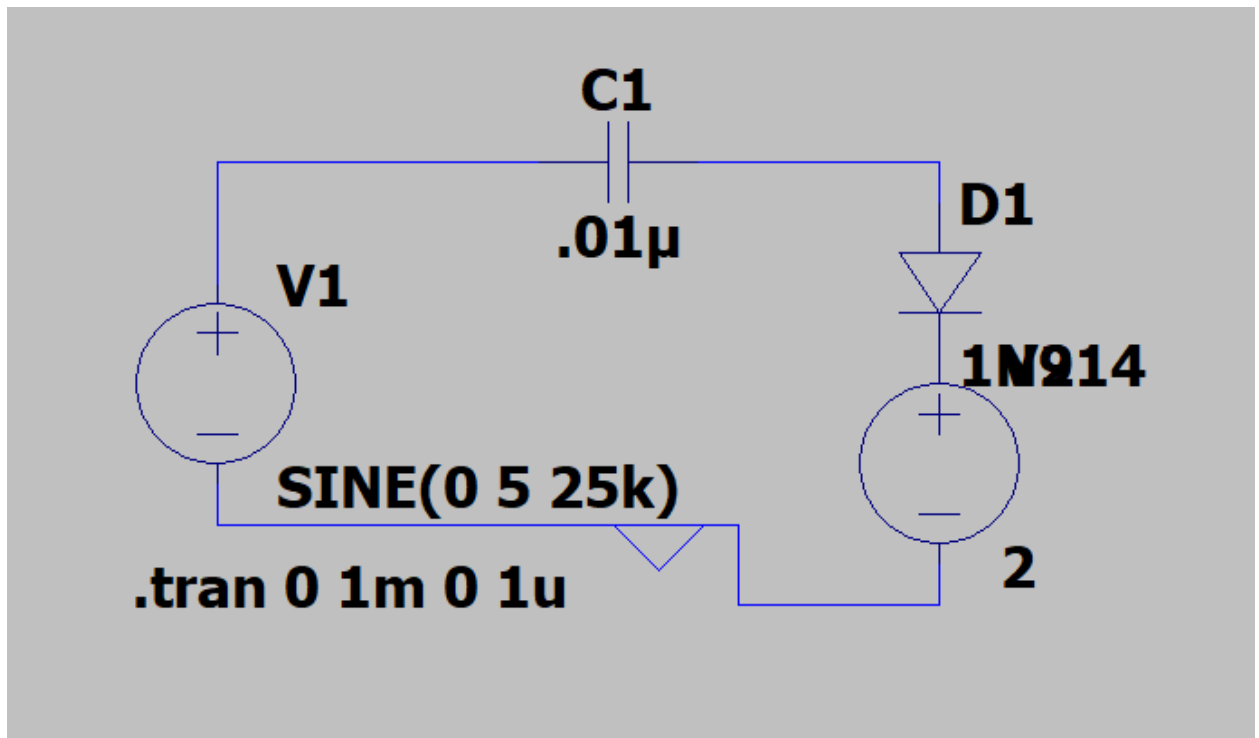


Waveform:

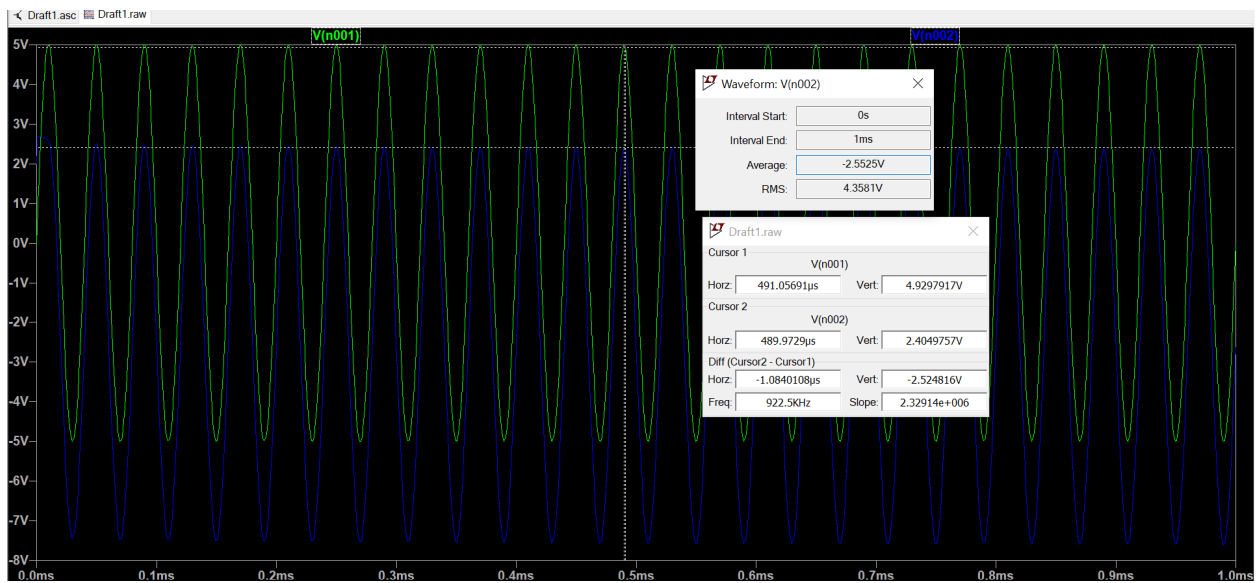


Peak value : 2.40V

Avg value: -2.55V

4) Circuit :

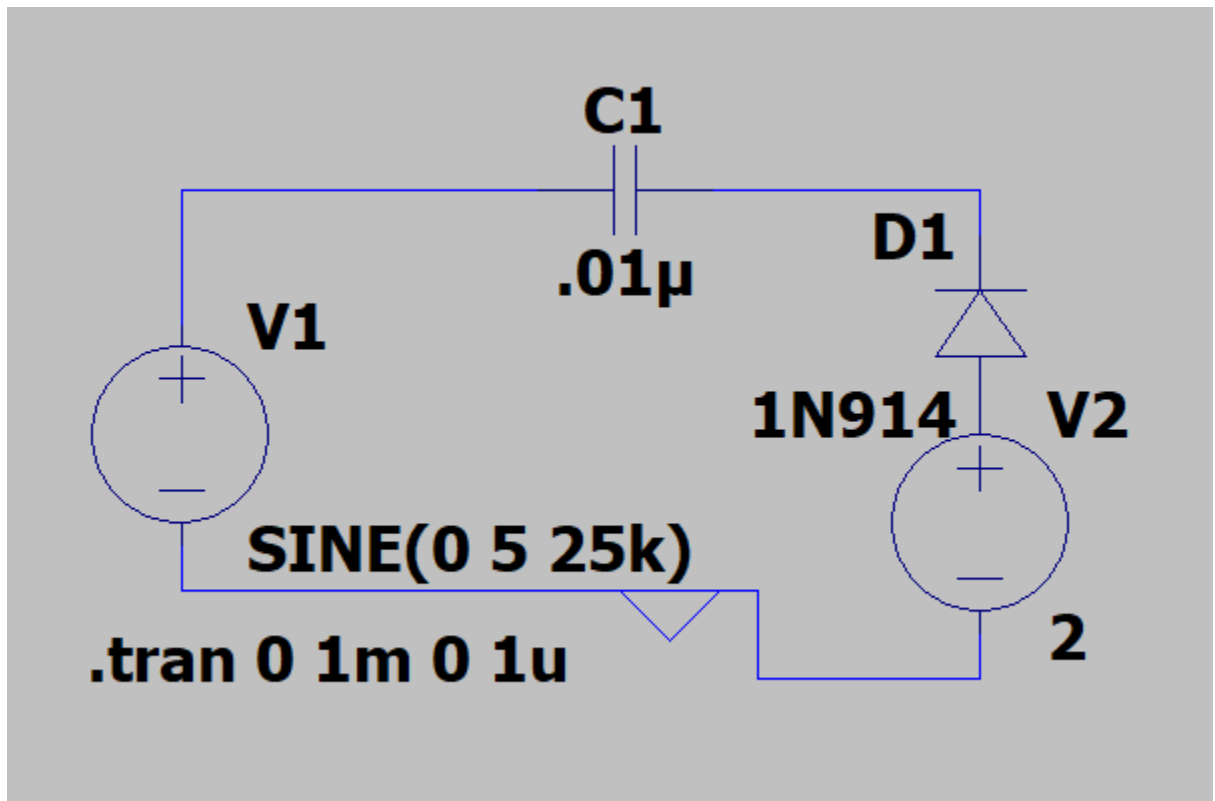

Waveform:

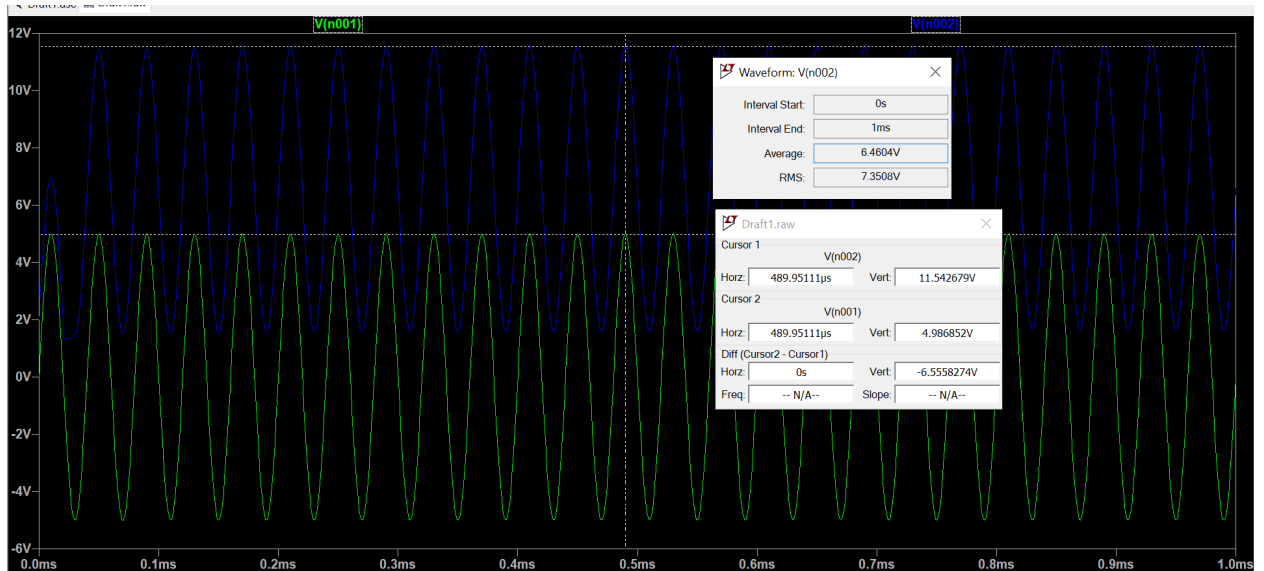

Peak value : 11.54V

Avg value: 6.46V

Observations:

1) Half wave rectifier :

- They only give either the positive or negative voltage output depending on the orientation of the diode
- When a 100 μ F capacitor is connected in parallel with the resistor , it takes some time to be fully charged but after that it reduces the ripples in the circuit and circuit almost reaches a steady DC state
- When a 0.1 μ F capacitor is connected in parallel with the resistor , it quickly becomes fully charged but as it stores less energy it is not able to maintain the steady DC state for long
- When a 0.1 μ F capacitor is connected in parallel with the resistor and frequency is increased to 25kHz, the DC output is a lot steady and the ripples are greatly reduced.(i.e. On increasing frequency the ripples are reduced)

2) Diode clipping circuit:

- This circuit is used to remove (clip) a part of the waveform from the input and the clipped part is based on the orientation of the diode and the DC voltage source connected to it.

3) Diode clamping circuit:

- It is used to shift the wave either in upward or downward direction based on the orientation of the diode and the voltage source connected to it
- If the output terminal of the diode is connected to the capacitor then the waveform shifts in the positive direction , and if the input terminal of the diode is connected to the capacitor then the waveform shifts towards negative direction.
- If the positive terminal of the voltage source is connected to the ground then the waveform shifts in the negative direction , and if the negative terminal of the voltage source is connected to the ground then the waveform shifts in the positive direction.

Applications :

1) Half wave rectifier :

- They are used in low power simple battery charger circuits
- They are used in pulse generator circuits.

2) Diode clipping circuit:

- They are used for the protection of transistors from transients
- They can be used as voltage limiters and amplitude selectors

3) Diode clamping circuit:

- They can be used as voltage doublers or voltage multipliers
 - They can be used for removing distortions.
-