

**ECE113|BASIC ELECTRONICS**

**Dr. S.S.Jamuar**

**Lab\_4:**

**Student Name : Shivam Agarwal**

**Roll No. : 2020123**

**Date : 11/7/2021**


---

**AIM 1 : Observing the step response of the RLC circuit and obtaining the period of oscillation, time constant and peak overshoot and comparing it with theoretical value**

**Components Used :** voltage source ,resistor ,inductor, capacitor , wires.

**Software used :** LTspice

**Undamped natural frequency:**

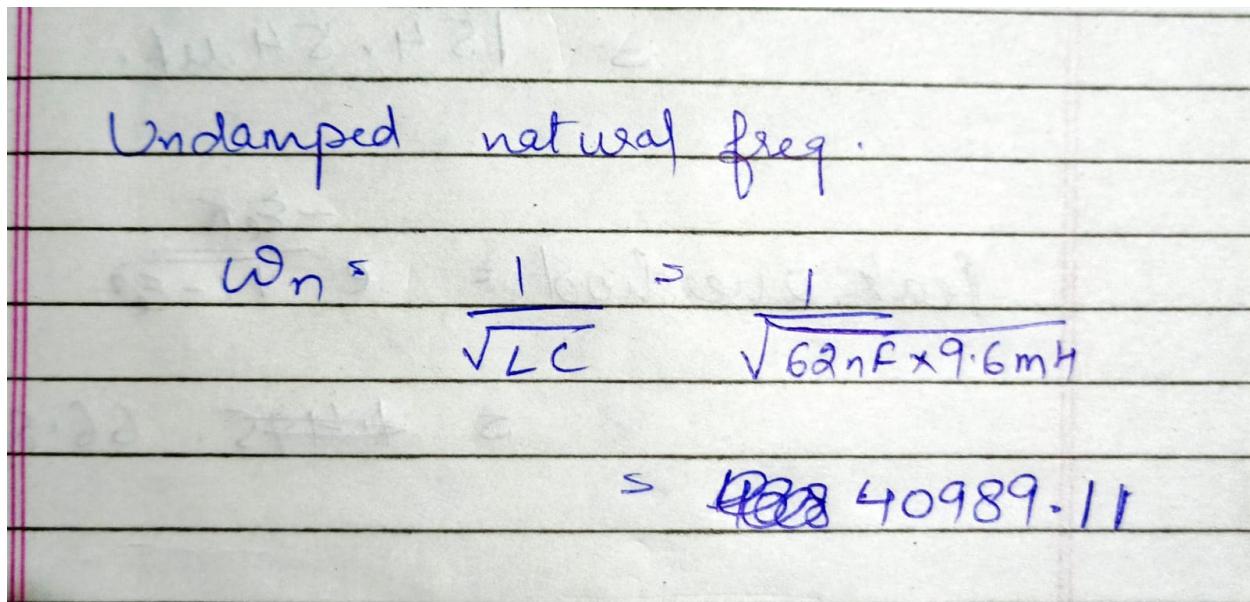

Undamped natural freq.

$$\omega_n = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{62nF \times 9.6mH}}$$
$$\Rightarrow 40989.11$$

### Critical resistance :

Critical resistance →

So Damping factor = 1

$$E_c = R/2 \sqrt{\frac{C}{L}}$$

$$I = \frac{R}{2} \sqrt{\frac{62 \text{nF}}{9.6 \text{mH}}}$$

$$R = 2 \sqrt{\frac{9.6 \text{mH}}{62 \text{nF}}}.$$


$$= 787 \Omega.$$

~~= 787 Ω~~


Hence  $R = \text{Resistor} + \text{R inductor}$

$$\text{Resistor} = R - 50 \\ = 737 \Omega.$$

## Waveform :

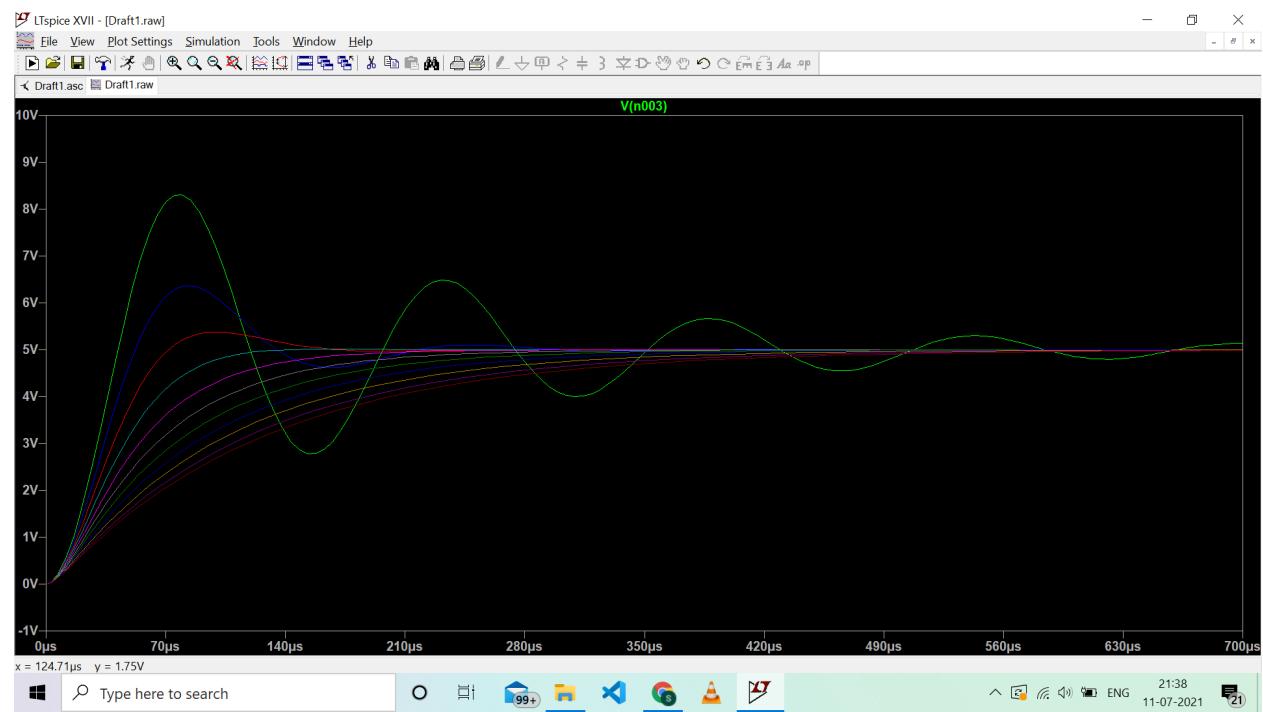

## Circuit Diagram

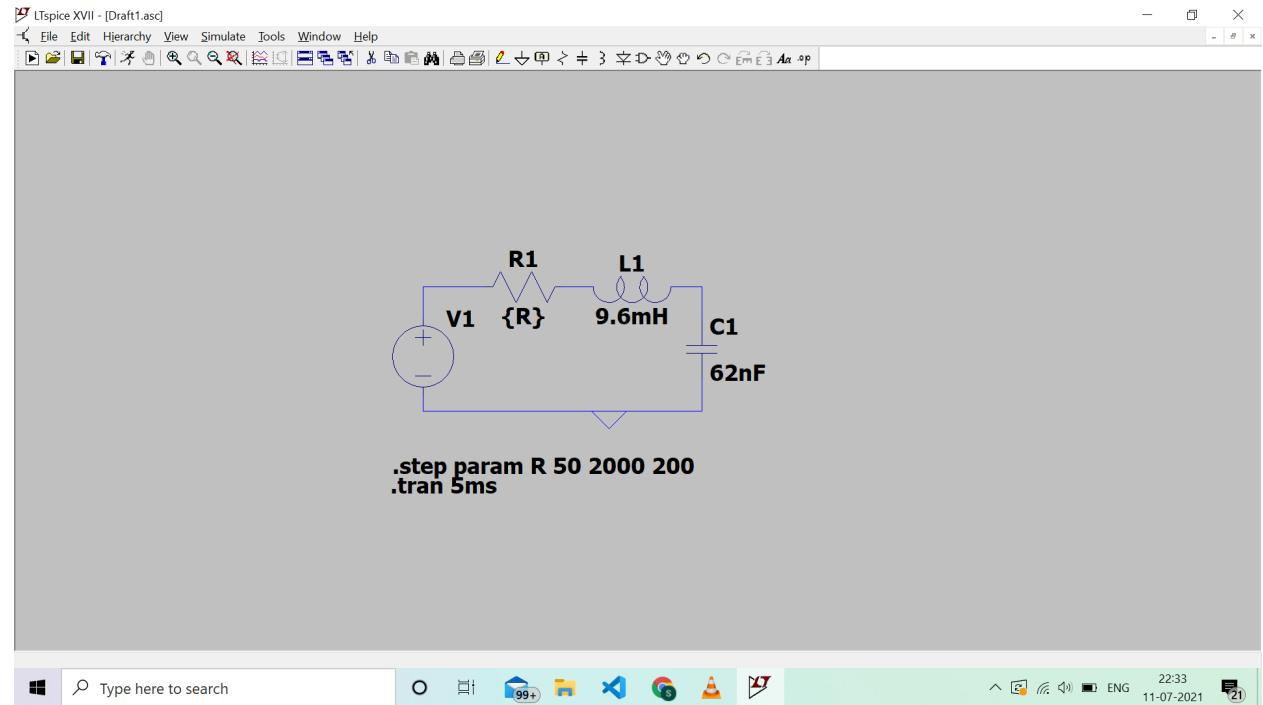

### Theoretical calculations (for different values of R) :

1) For  $R = 50 \text{ ohm}$

$$\text{For } R = 50 \Omega.$$

$$\text{so } R_{\text{eq}} = 50 + 50 = 100 \Omega.$$

$$\text{Damping factor} = \frac{R_{\text{eq}}}{2} \sqrt{\frac{C}{L}}$$

$$= 0.127.$$

$$\text{Time Period} = \frac{2\pi}{\omega_n \sqrt{1 - \xi_e^2}}$$

$$= \frac{2\pi}{40989.11 \sqrt{1 - 0.127^2}}$$

$$= 154.54 \mu\text{s}.$$

$$\text{Peak overshoot} = e^{-\frac{\pi}{\sqrt{1-\xi_e^2}}}$$

$$M_p = e^{\frac{-\pi(0.127)}{\sqrt{1-0.127^2}}}$$

$$= 0.6688$$

$$M_p\% = 66.88\%$$

$$\text{Time constant} = \frac{2L}{R_{\text{eq}}}$$

$$= \frac{2 \times 9.6 \times 1}{100}$$

$$= 192 \mu\text{s}$$

2) For  $R = 250 \Omega$

For  $R = 250 \Omega$ .

$$R_{eq} = 300 \Omega$$

$$\omega_n = \frac{300}{2} \sqrt{\frac{C}{L}}$$
$$\Rightarrow 0.381$$

$$\text{Time period} = \frac{2\pi}{\omega_n \sqrt{1 - \xi_e^2}}$$

$$= \frac{2\pi}{40989.11 \sqrt{1 - 0.381^2}}$$
$$= 165 \mu s$$

$$\text{Peak overshoot} = e^{-\frac{2\zeta\pi}{1-\xi^2}}$$
$$= 0.274$$

$$M_p\% = 27.4\%$$

$$\text{Time constant} = \frac{2L}{R_{eq}}$$

$$= \frac{2 \times 9.6 \times 10^{-3}}{300}$$
$$= 64 \mu s$$

3) For  $R = 450 \text{ ohm}$

$$\text{for } R = 450 \Omega$$

$$R_{\text{eq}} = 500 \Omega$$

$$E_0 = \frac{500}{2} \sqrt{\frac{C}{L}}$$

$$= 0.635$$

$$\text{Time period} = \frac{2\pi}{\omega_n \sqrt{1 - E_0^2}}$$

$$= \frac{2\pi}{40889.11 \sqrt{1 - 0.635^2}}$$

$$= 198.42 \mu\text{s}$$

$$\text{Peak overshoot} = e^{-\frac{\pi E_0}{\sqrt{1 - E_0^2}}}$$

$$= 0.0756$$

$$M_p\% = 7.56\%$$

$$\text{Time constant} = \frac{2L}{R_{\text{eq}}}$$


$$= \frac{2 \times 9.6 \times 10^{-3}}{500}$$

$$= \frac{19.2}{5}$$


$$= 3.84 \mu\text{s}$$

## Practical observations:

1) For 50 ohm resistance:

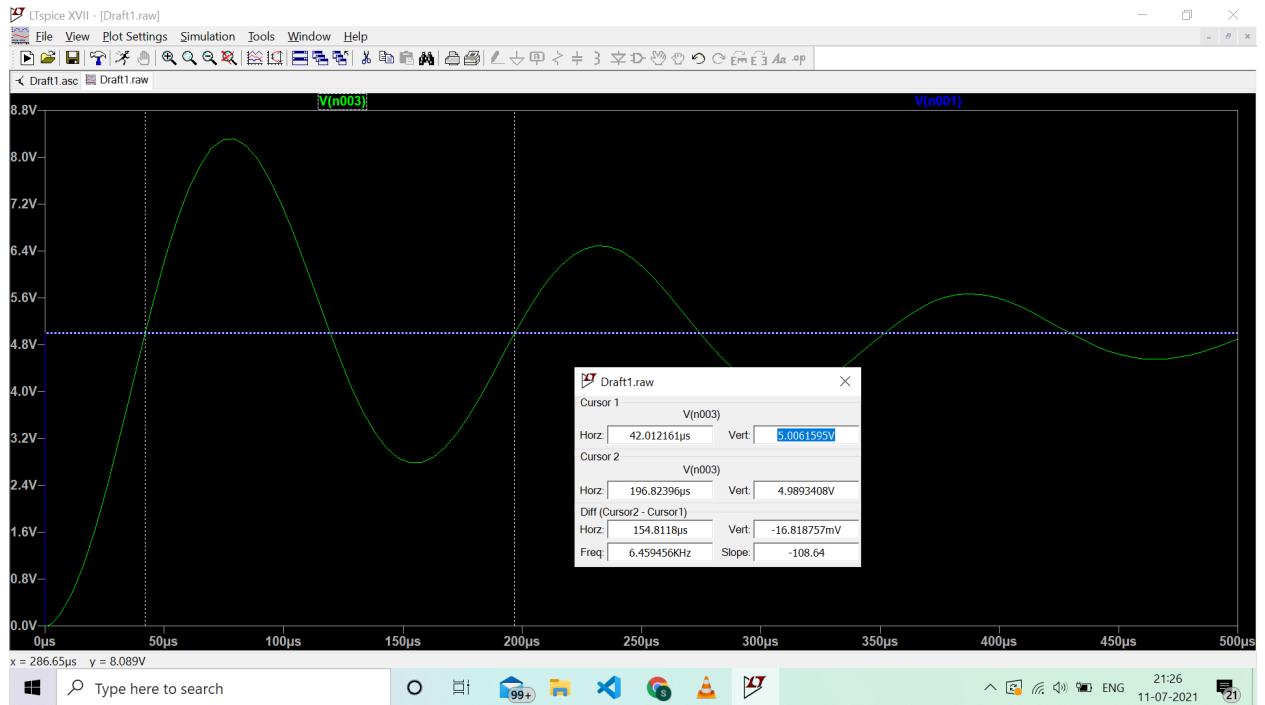


Time period = 154.81μs

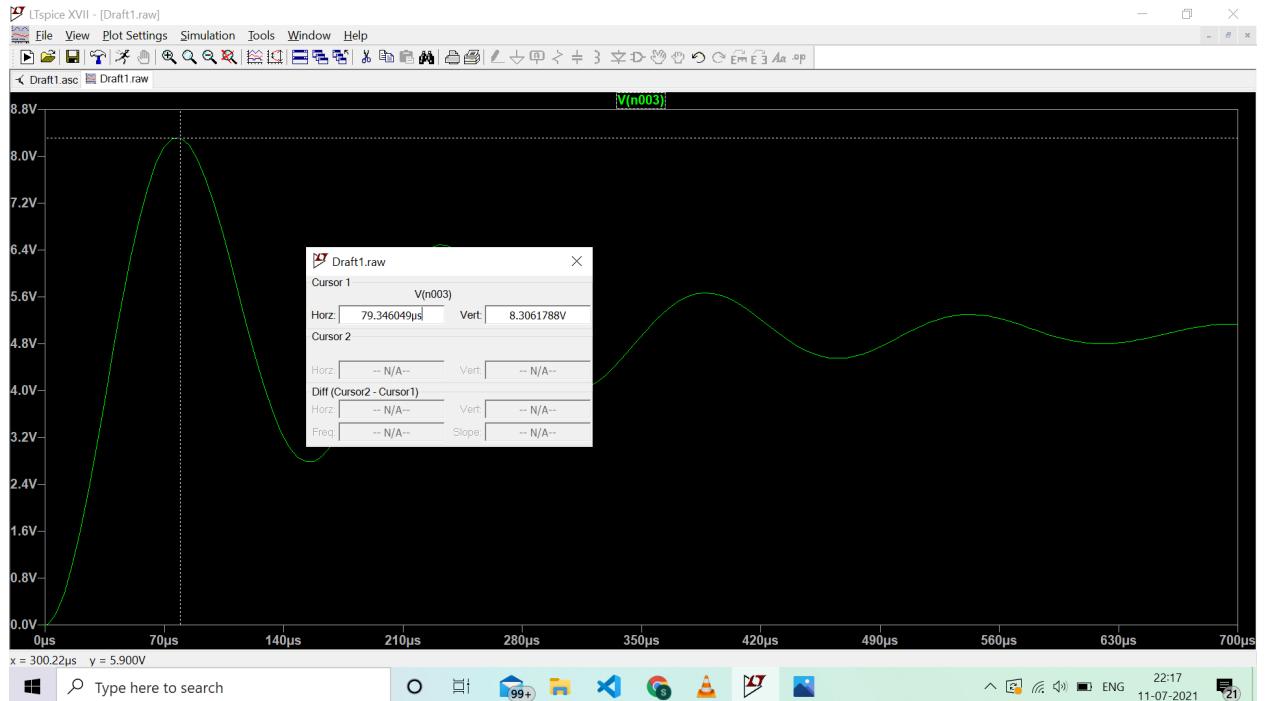


$$\text{Peak overshoot} = \frac{(8.306 - 5)}{5}$$

$$= 66.12\%$$

## 2) For R = 250 ohm

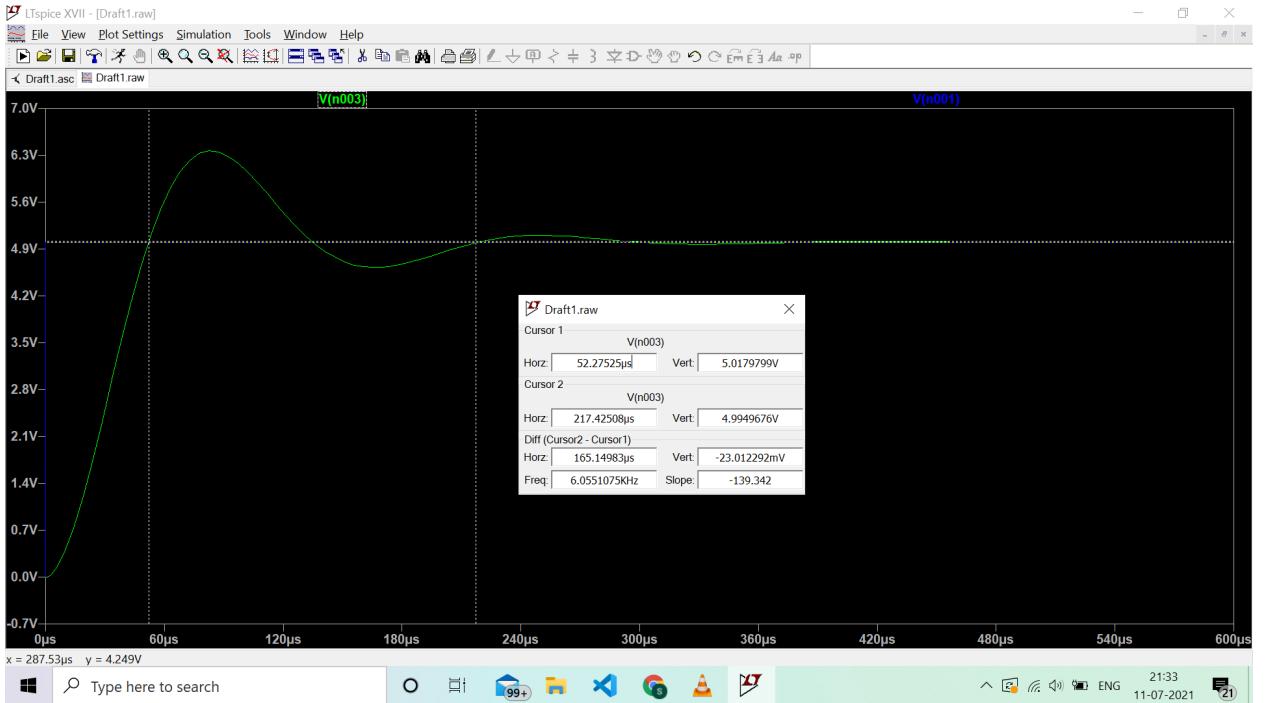


Time period = 165.14µs

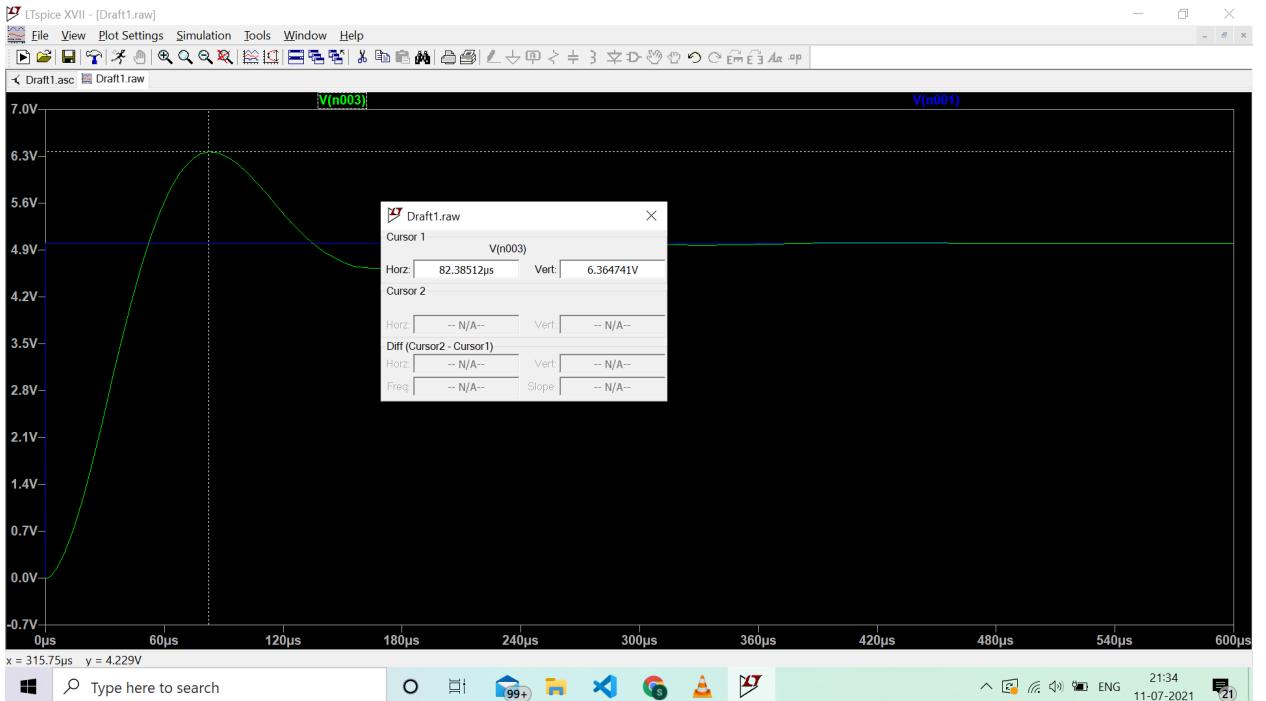


$$\text{Peak overshoot} = \frac{(6.364 - 5)}{5}$$

$$= 27.28\%$$

### 3) For R = 450 ohm

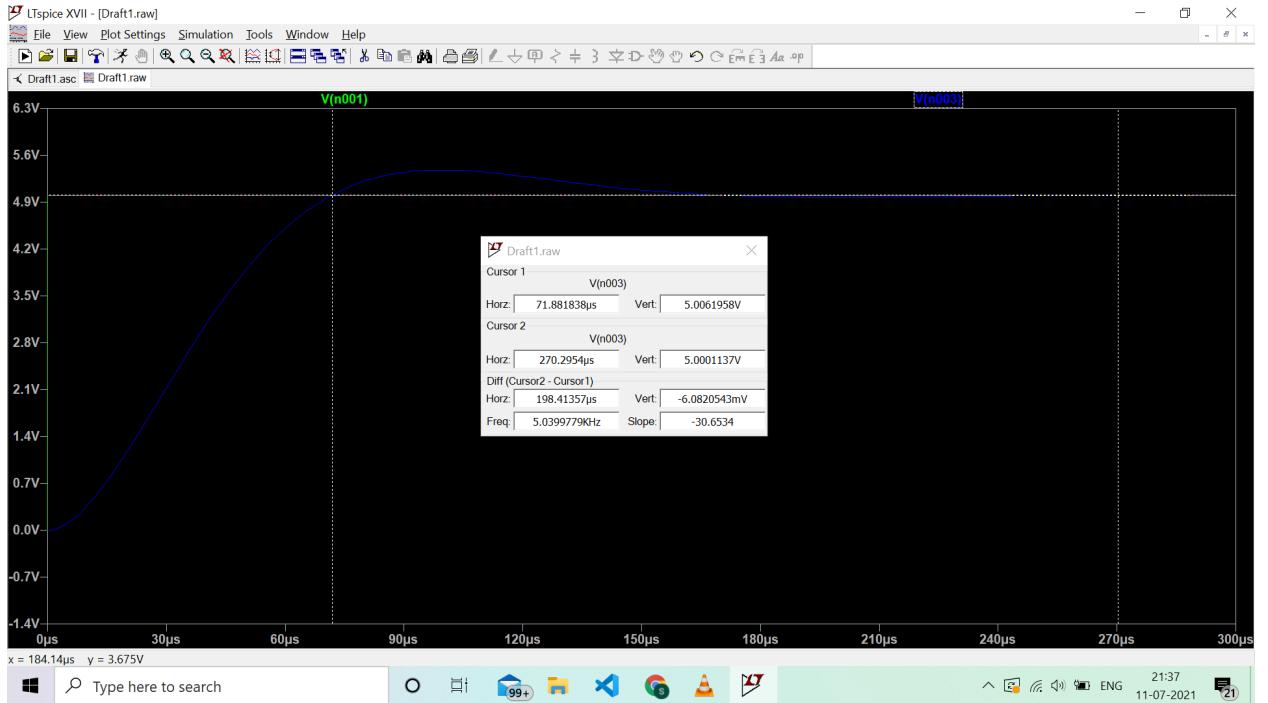

Time period = 198.41μs

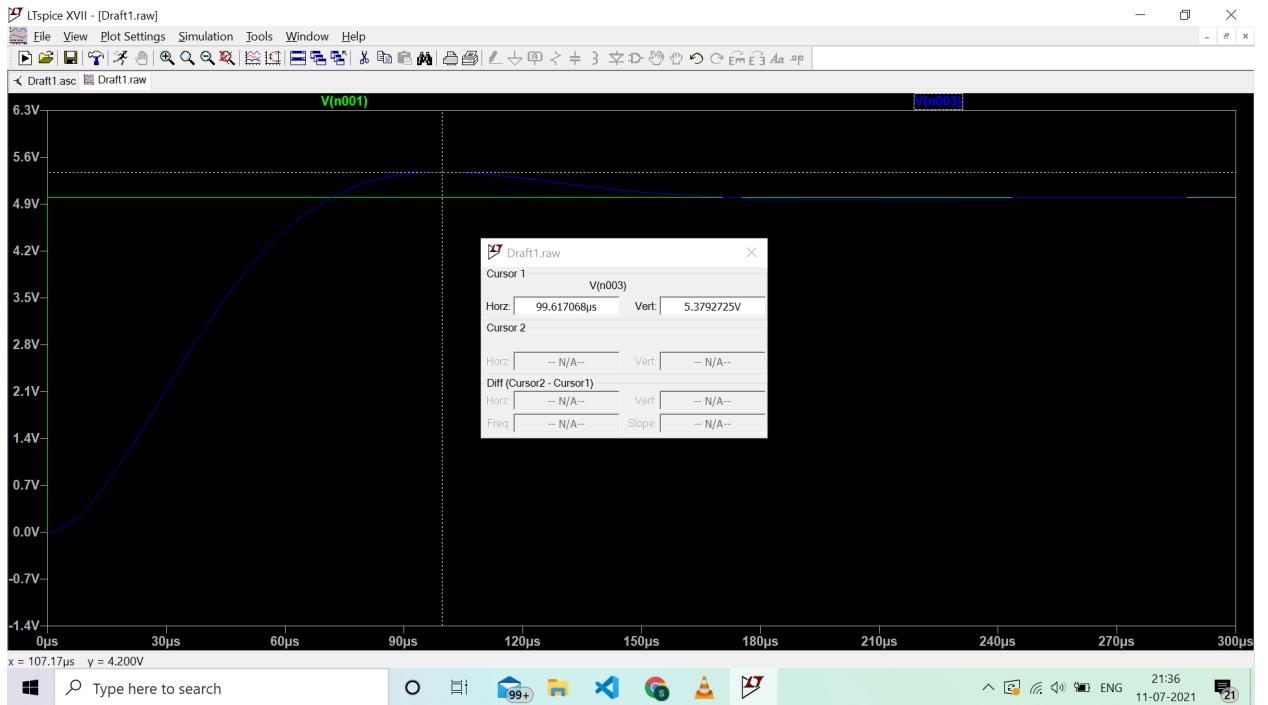

### **Observations :**

S. No.	R (ohm)	R <sub>eq</sub> (ohm)	Theoretical values			Experimental values	
			Time Period (μs)	Peak Oversh- oot (in %)	Time constant(μs)	Time Period (μs)	Peak Oversh- oot (in %)
1	50	100	154.54	66.88	192	154.81	66.12
2	250	300	165	27.4	64	165.14	27.28
3	450	500	198.42	7.56	38.4	198.41	7.58

### **Applications :**

1. RLC circuits have many applications as oscillator circuits.
  2. They are used in television sets and radio receivers for tuning purposes.
-